

10.1.2 Magnetic circuits

Uniform flux and magnetic field inside a rectangular element:

MMF between ends of element is

$$\mathcal{F} = H\ell$$


Since $H = B / \mu$ and $B = \Phi / A_c$, we can express \mathcal{F} as

$$\mathcal{F} = \Phi \mathcal{R}$$

with

$$\mathcal{R} = \frac{\ell}{\mu A_c}$$

A corresponding model:

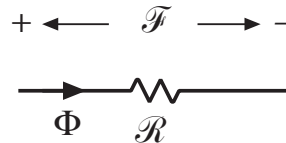

\mathcal{R} = reluctance of element

Magnetic circuits: magnetic structures composed of multiple windings and heterogeneous elements


- Represent each element with reluctance
- Windings are sources of MMF
- MMF \rightarrow voltage, flux \rightarrow current
- Solve magnetic circuit using Kirchoff's laws, etc.

Magnetic analog of Kirchoff's current law


Divergence of $\mathbf{B} = 0$

Flux lines are continuous
and cannot end

Total flux entering a node
must be zero

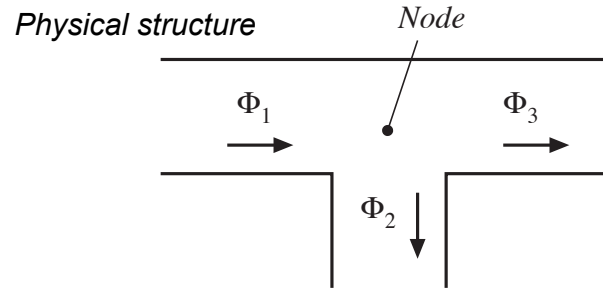

Magnetic circuit

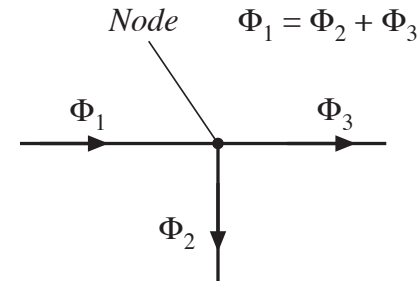

Magnetic analog of Kirchoff's voltage law

Follows from Ampere's law:


$$\oint_{\text{closed path}} \mathbf{H} \cdot d\boldsymbol{\ell} = \text{total current passing through interior of path}$$

Left-hand side: sum of MMF's across the reluctances around the closed path



Right-hand side: currents in windings are sources of MMF's. An n -turn winding carrying current $i(t)$ is modeled as an MMF (voltage) source, of value $ni(t)$.

Total MMF's around the closed path add up to zero.

Example: inductor with air gap

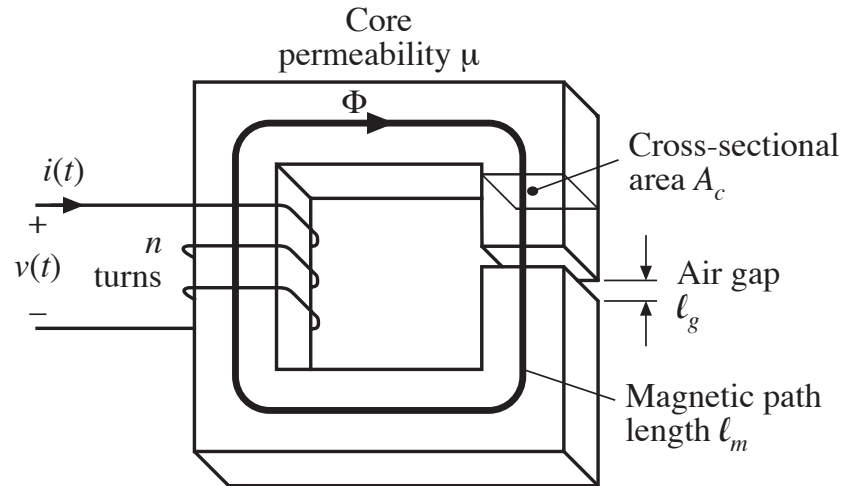

Magnetic circuit model

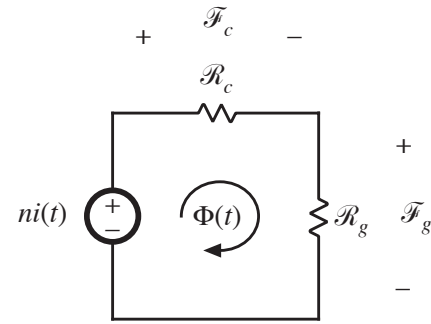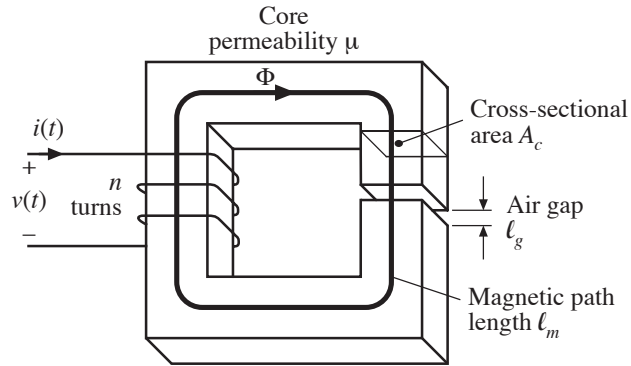


$$\mathcal{F}_c + \mathcal{F}_g = ni$$

$$ni = \Phi (\mathcal{R}_c + \mathcal{R}_g)$$

$$\mathcal{R}_c = \frac{\ell_c}{\mu A_c}$$

$$\mathcal{R}_g = \frac{\ell_g}{\mu_0 A_c}$$

Solution of model

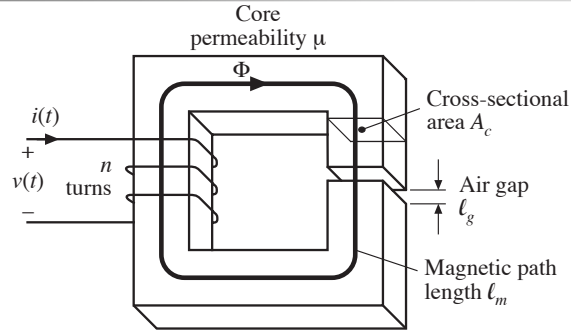


Faraday's law:
$$v(t) = n \frac{d\Phi(t)}{dt}$$

Substitute for Φ :
$$v(t) = \frac{n^2}{\mathcal{R}_c + \mathcal{R}_g} \frac{di(t)}{dt}$$

Hence inductance is
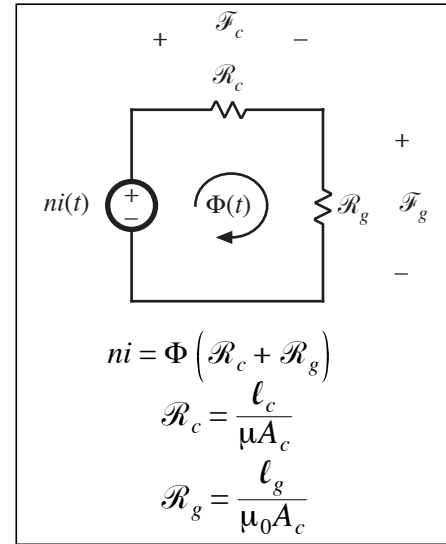
$$L = \frac{n^2}{\mathcal{R}_c + \mathcal{R}_g}$$



Effect of air gap

$$ni = \Phi (\mathcal{R}_c + \mathcal{R}_g)$$

$$L = \frac{n^2}{\mathcal{R}_c + \mathcal{R}_g}$$

$$\Phi_{sat} = B_{sat} A_c$$

$$I_{sat} = \frac{B_{sat} A_c}{n} (\mathcal{R}_c + \mathcal{R}_g)$$

Effect of air gap:

- decrease inductance
- increase saturation current
- inductance is less dependent on core permeability

