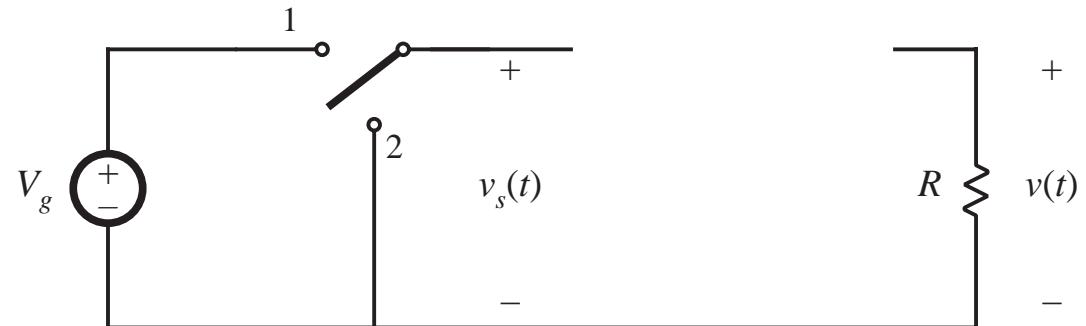


2.1 Introduction Buck converter


SPDT switch changes dc component




Switch output voltage waveform

Duty cycle D :
 $0 \leq D \leq 1$

complement D' :
 $D' = 1 - D$

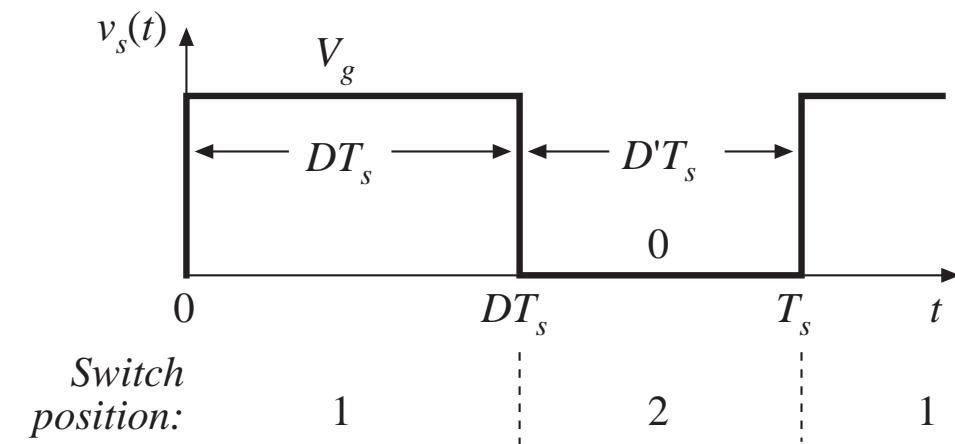

Dc component of switch output voltage

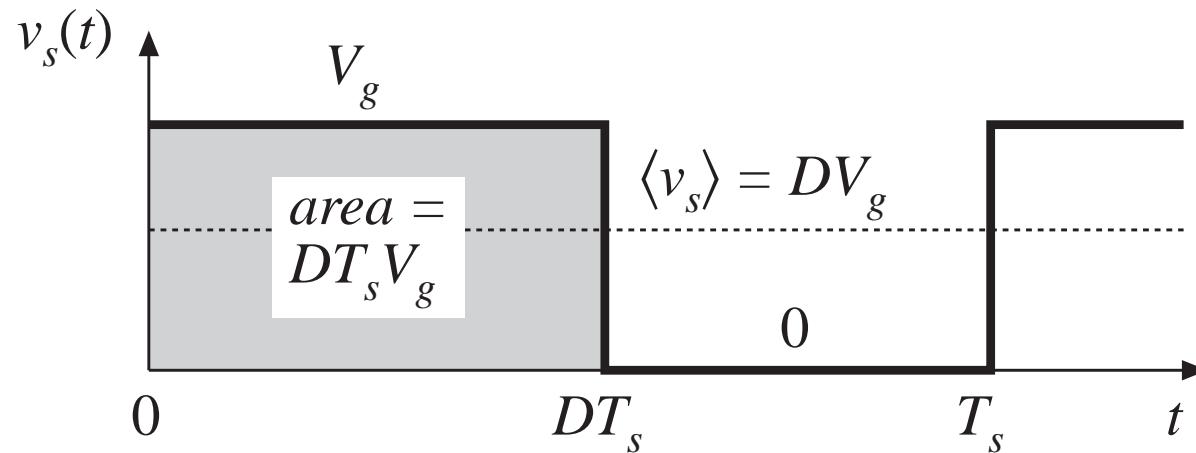


Fourier analysis: Dc component = average value


$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$

$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$

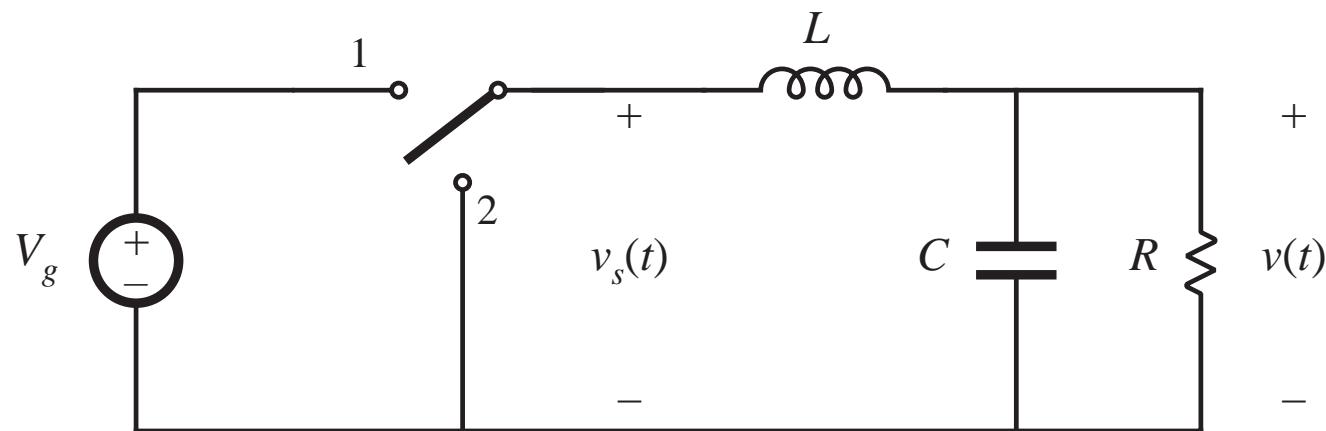Insertion of low-pass filter to remove switching harmonics and pass only dc component





$$v \approx \langle v_s \rangle = DV_g$$


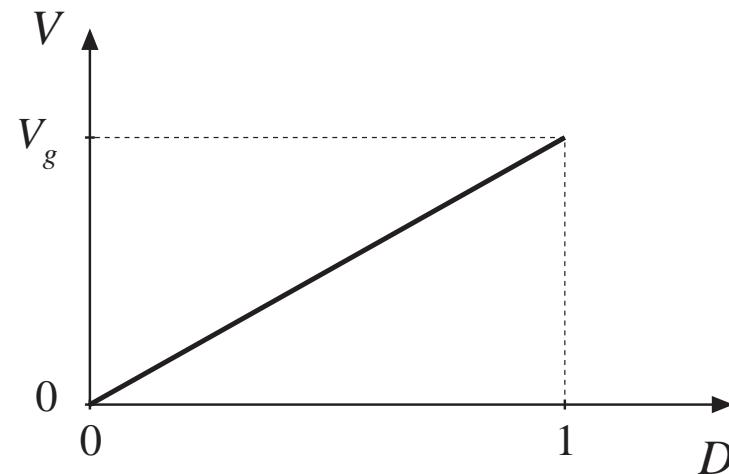


Three basic dc-dc converters



Buck

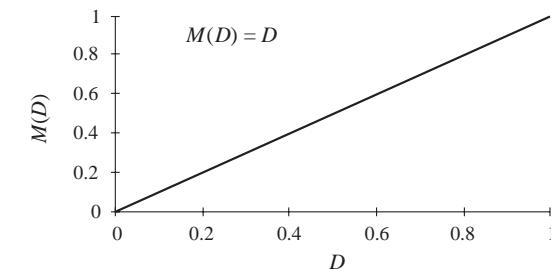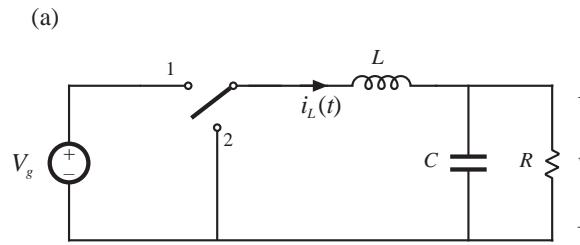

Boost

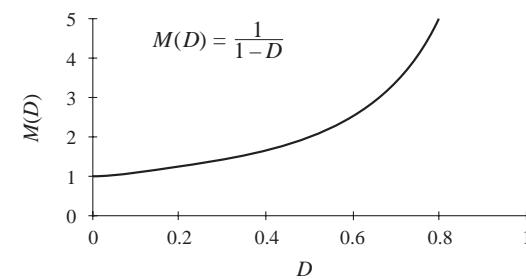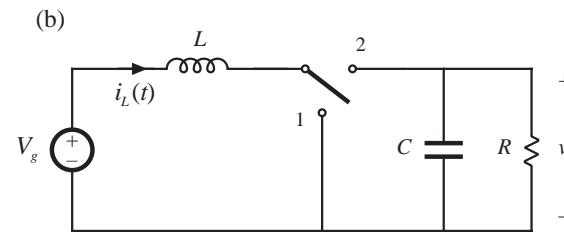

Buck-boost

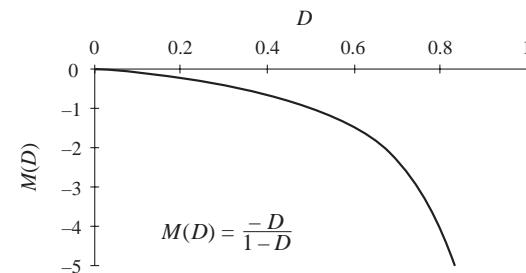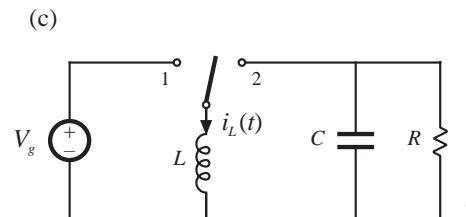

Objectives of this chapter

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples