
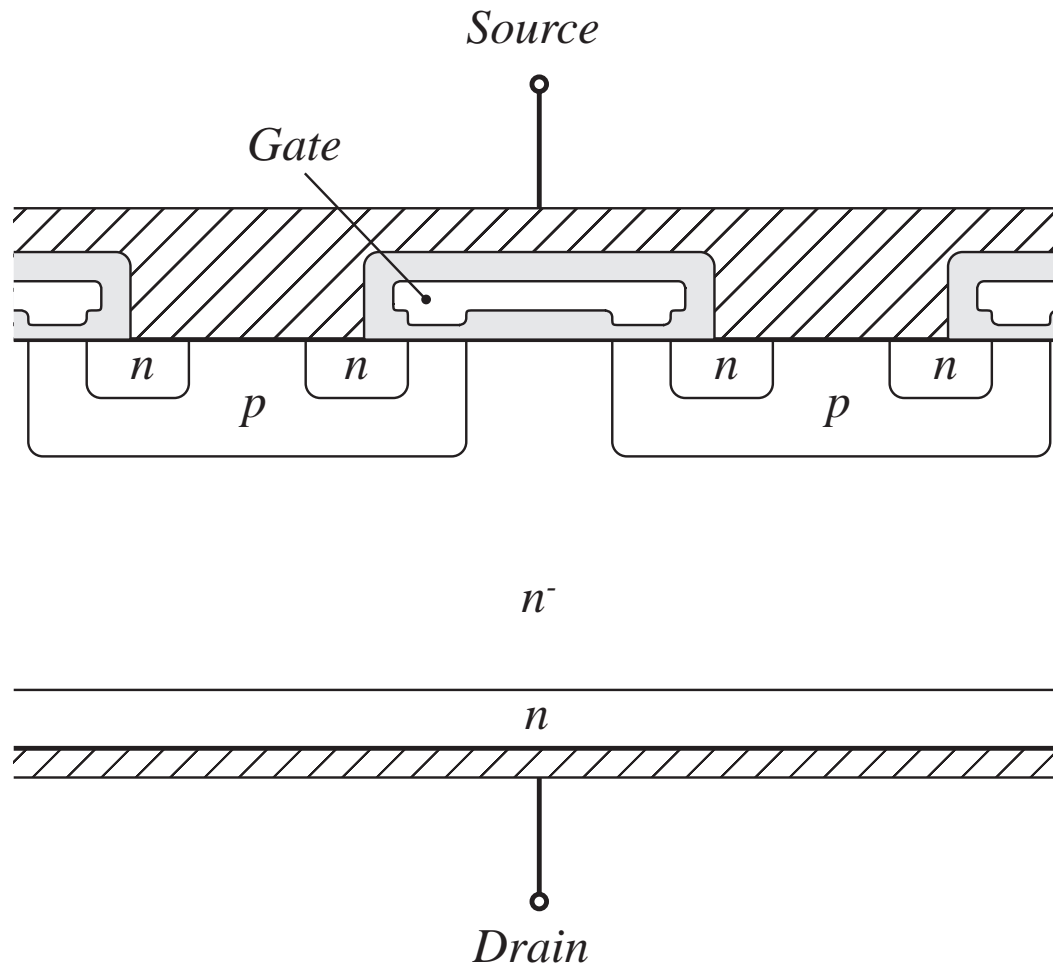


4.2.2. The Power MOSFET

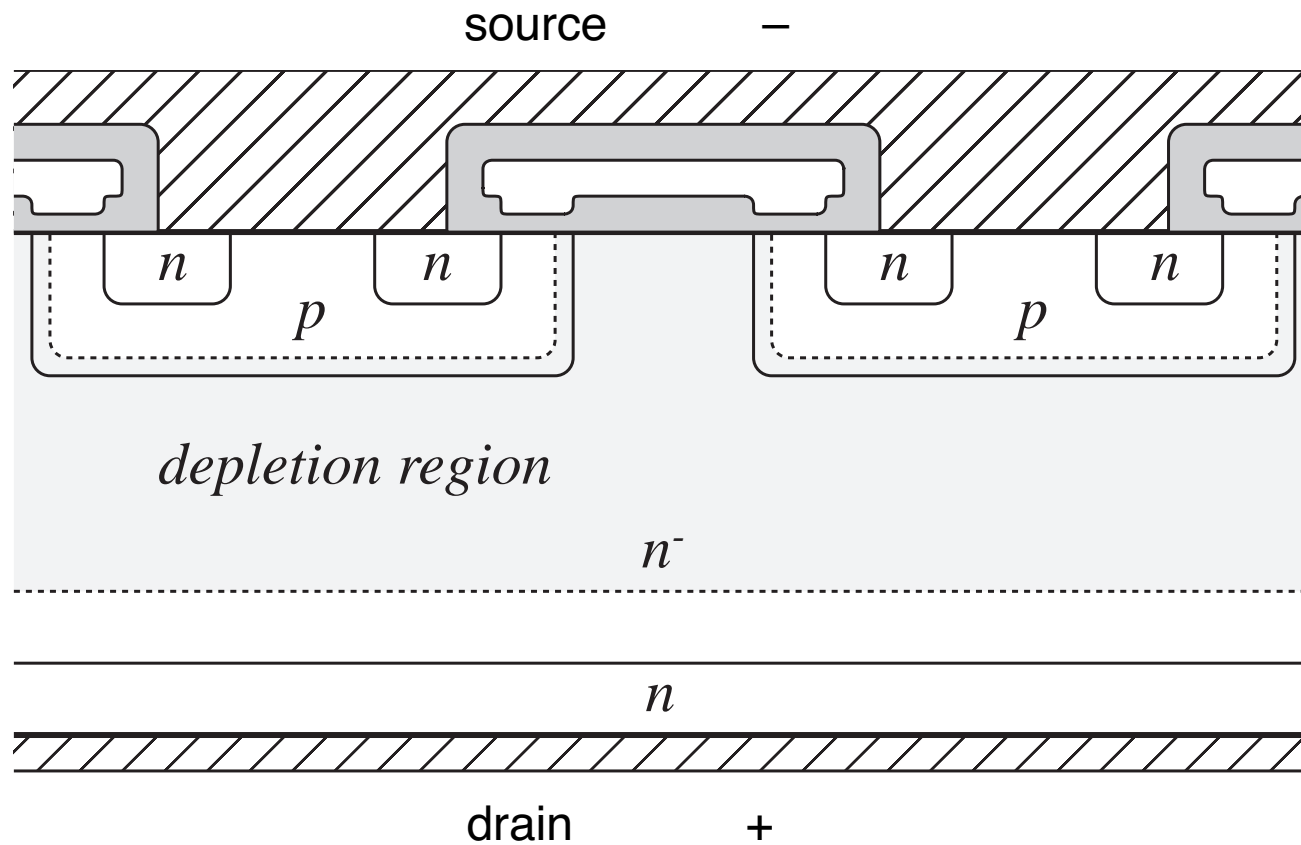


- Gate lengths approaching one micron
- Consists of many small enhancement-mode parallel-connected MOSFET cells, covering the surface of the silicon wafer
- Vertical current flow
- n-channel device is shown

MOSFET: Off state




- $p-n$ junction is reverse-biased
- off-state voltage appears across n^- region

MOSFET: on state

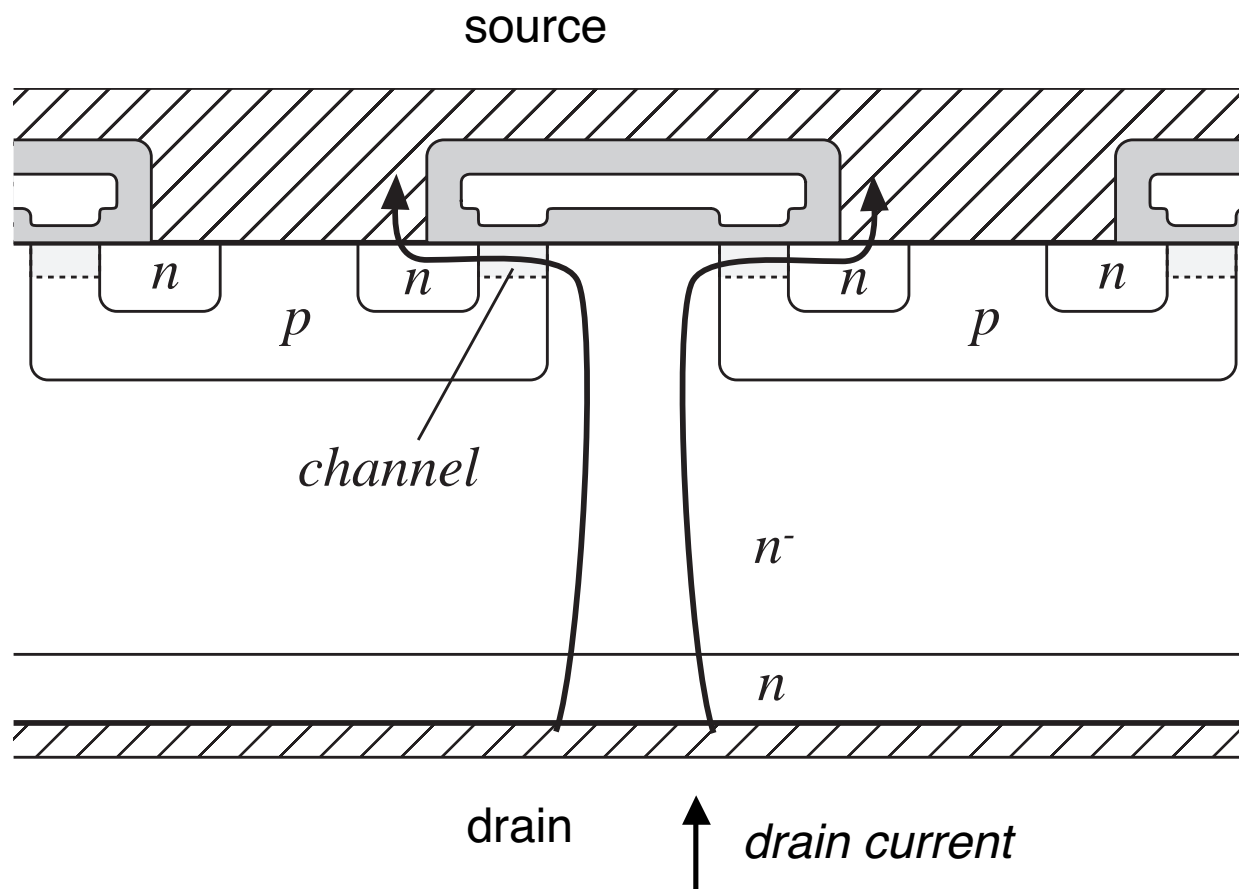


- p - n junction is slightly reverse-biased
- positive gate voltage induces conducting channel
- drain current flows through n region and conducting channel
- on resistance = total resistances of n region, conducting channel, source and drain contacts, etc.

MOSFET body diode

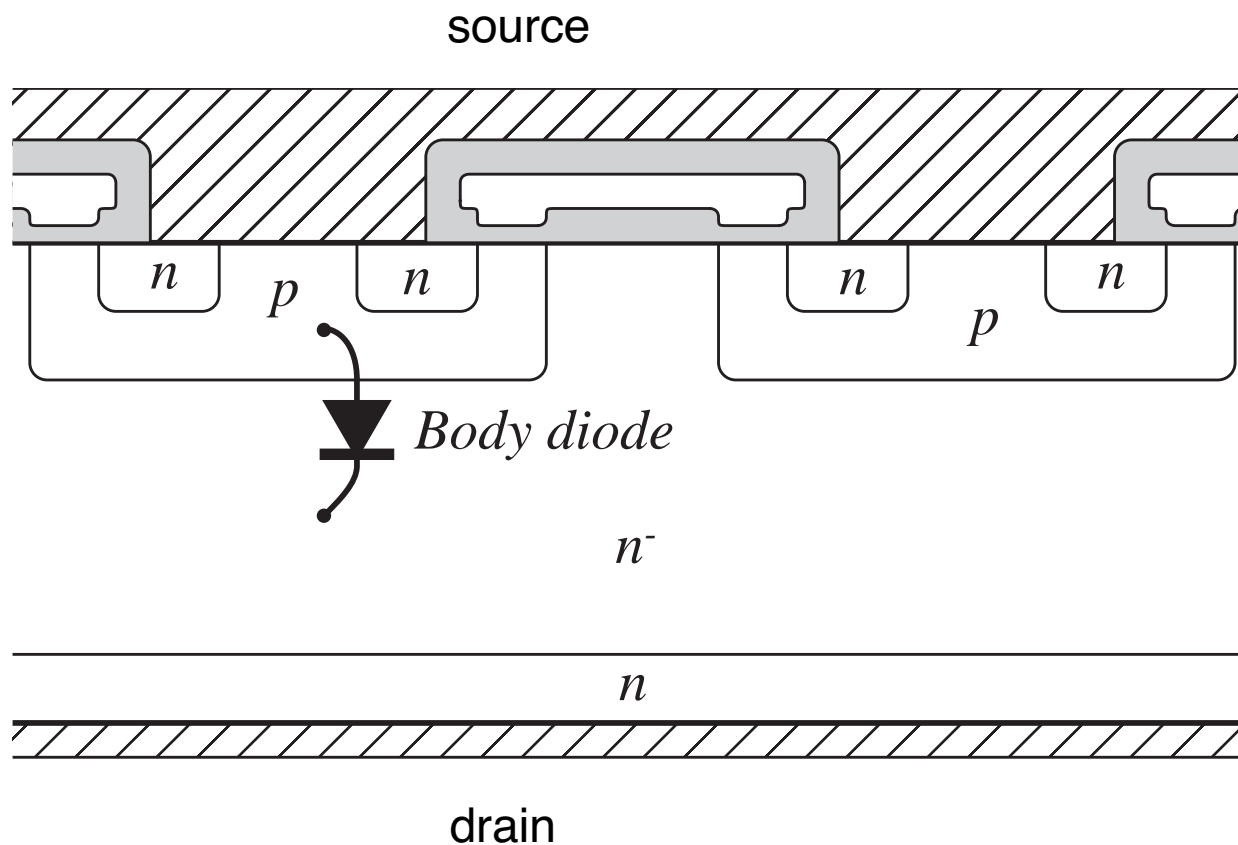


- p - n junction forms an effective diode, in parallel with the channel
- negative drain-to-source voltage can forward-bias the body diode
- diode can conduct the full MOSFET rated current
- diode switching speed not optimized — body diode is slow, Q_r is large

Typical MOSFET characteristics

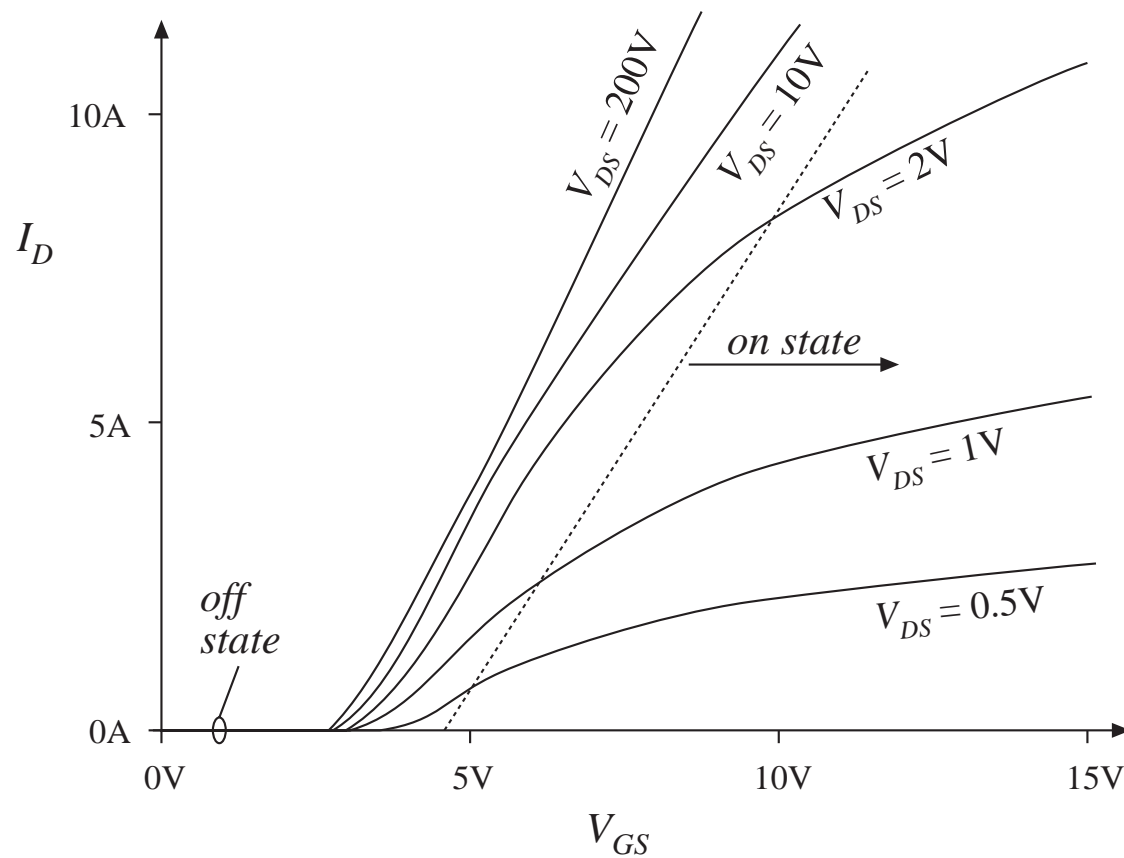

- Off state: $V_{GS} < V_{th}$
- On state: $V_{GS} \gg V_{th}$
- MOSFET can conduct peak currents well in excess of average current rating
— characteristics are unchanged
- on-resistance has positive temperature coefficient, hence easy to parallel

A simple MOSFET equivalent circuit

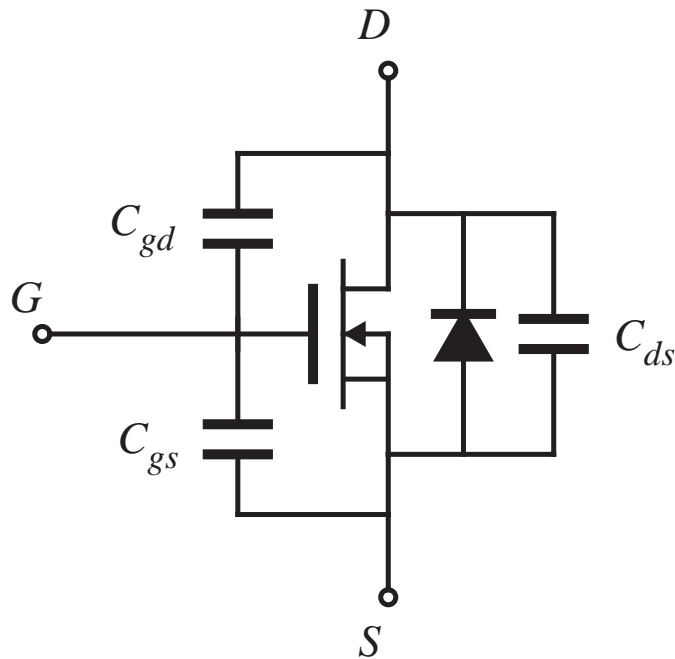


- C_{gs} : large, essentially constant
- C_{gd} : small, highly nonlinear
- C_{ds} : intermediate in value, highly nonlinear
- switching times determined by rate at which gate driver charges/discharges C_{gs} and C_{gd}

$$C_{ds}(v_{ds}) = \frac{C_0}{\sqrt{1 + \frac{v_{ds}}{V_0}}}$$

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C'_0}{\sqrt{v_{ds}}}$$

Switching loss caused by semiconductor output capacitances

Buck converter example

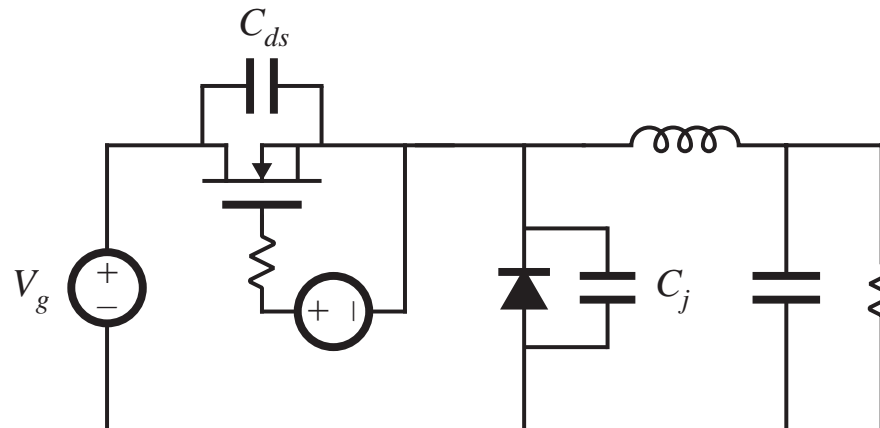

Energy lost during MOSFET turn-on transition
(assuming linear capacitances):

$$W_C = \frac{1}{2} (C_{ds} + C_j) V_g^2$$

MOSFET nonlinear C_{ds}

Approximate dependence of incremental C_{ds} on v_{ds} :

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C_0'}{\sqrt{v_{ds}}}$$

Energy stored in C_{ds} at $v_{ds} = V_{DS}$:

$$W_{Cds} = \int v_{ds} i_C dt = \int_0^{V_{DS}} v_{ds} C_{ds}(v_{ds}) dv_{ds}$$

$$W_{Cds} = \int_0^{V_{DS}} C_0'(v_{ds}) \sqrt{v_{ds}} dv_{ds} = \frac{2}{3} C_{ds}(V_{DS}) V_{DS}^2$$

— same energy loss as linear capacitor having value $\frac{4}{3} C_{ds}(V_{DS})$

Characteristics of several commercial power MOSFETs

<i>Part number</i>	<i>Rated max voltage</i>	<i>Rated avg current</i>	R_{on}	Q_g (typical)
IRFZ48	60V	50A	0.018 Ω	110nC
IRF510	100V	5.6A	0.54 Ω	8.3nC
IRF540	100V	28A	0.077 Ω	72nC
APT10M25BNR	100V	75A	0.025 Ω	171nC
IRF740	400V	10A	0.55 Ω	63nC
MTM15N40E	400V	15A	0.3 Ω	110nC
APT5025BN	500V	23A	0.25 Ω	83nC
APT1001RBNR	1000V	11A	1.0 Ω	150nC

MOSFET: conclusions

- A majority-carrier device: fast switching speed
- Typical switching frequencies: tens and hundreds of kHz
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V
- 1000V devices are available, but are useful only at low power levels (100W)
- Part number is selected on the basis of on-resistance rather than current rating