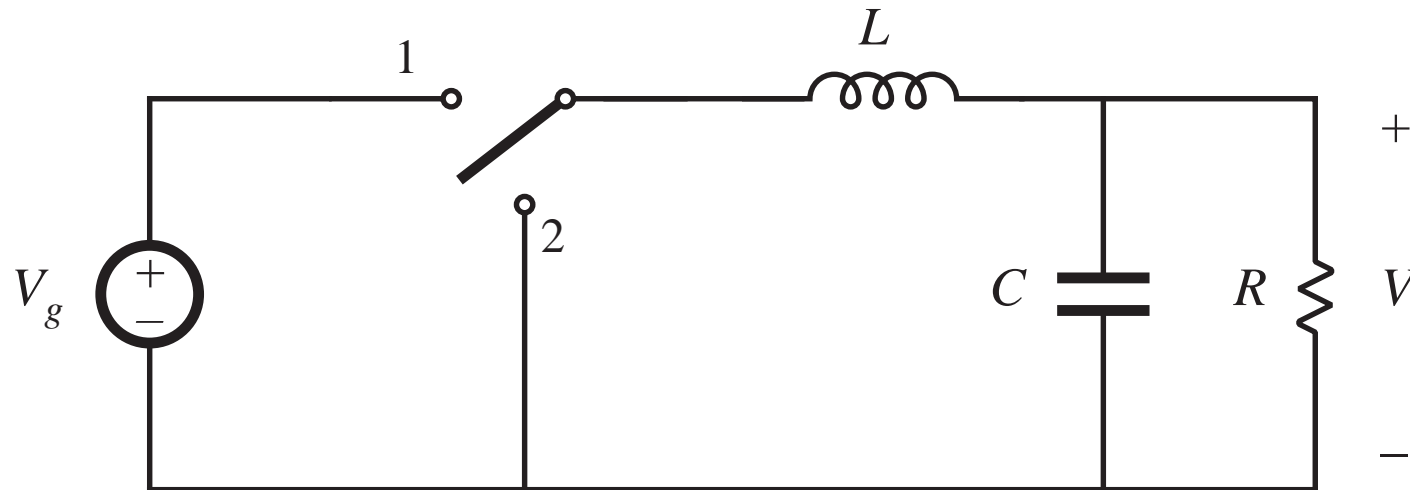


## 6.1. Circuit Manipulations

---



Begin with buck converter: derived in Chapter 1 from first principles


- Switch changes dc component, low-pass filter removes switching harmonics
- Conversion ratio is  $M = D$

## 6.1.1. Inversion of source and load

Interchange power input and output ports of a converter


Buck converter example

$$V_2 = DV_1$$

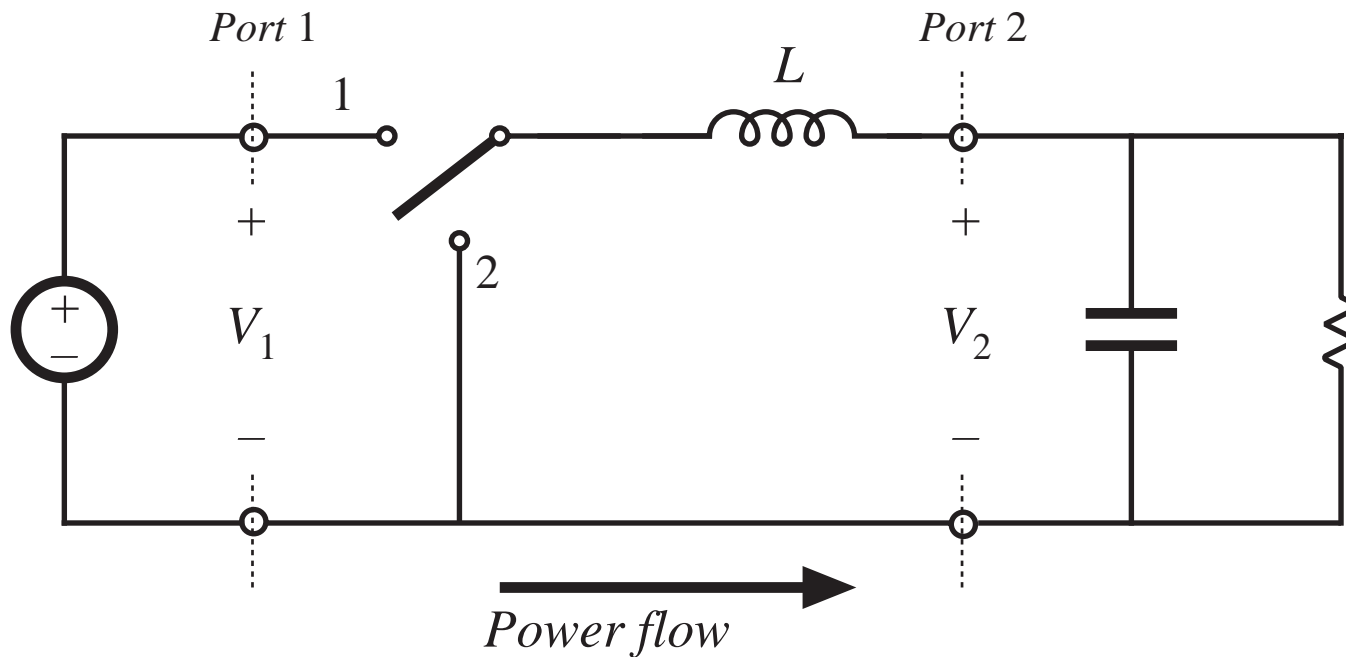

# Inversion of source and load

Interchange power source and load:

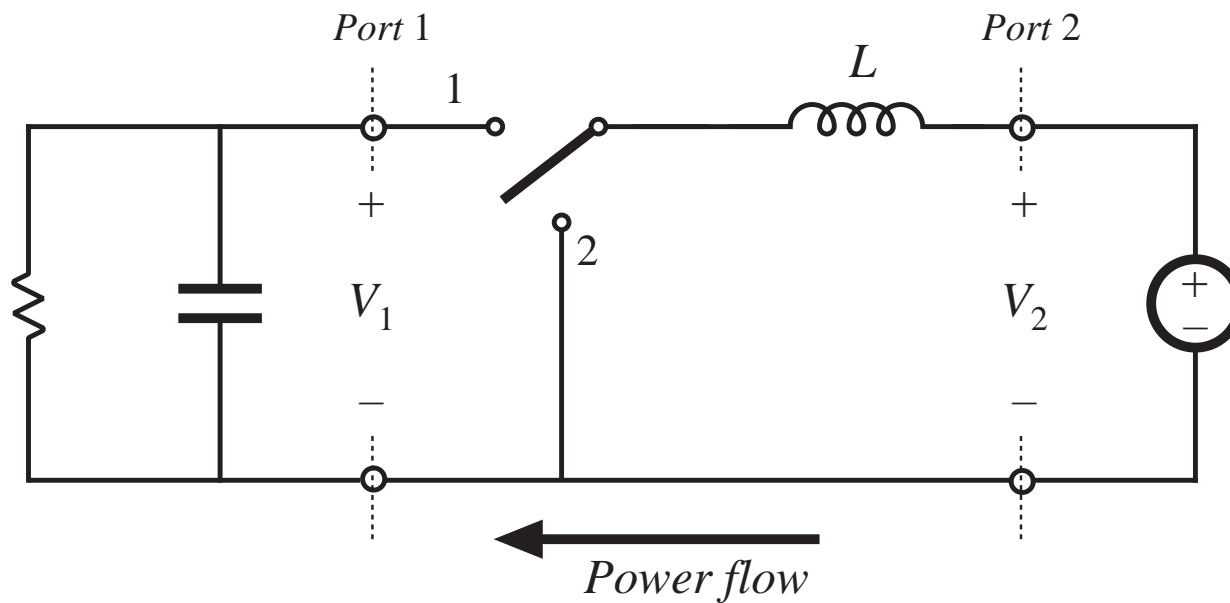


$$V_2 = DV_1$$

$$V_1 = \frac{1}{D} V_2$$
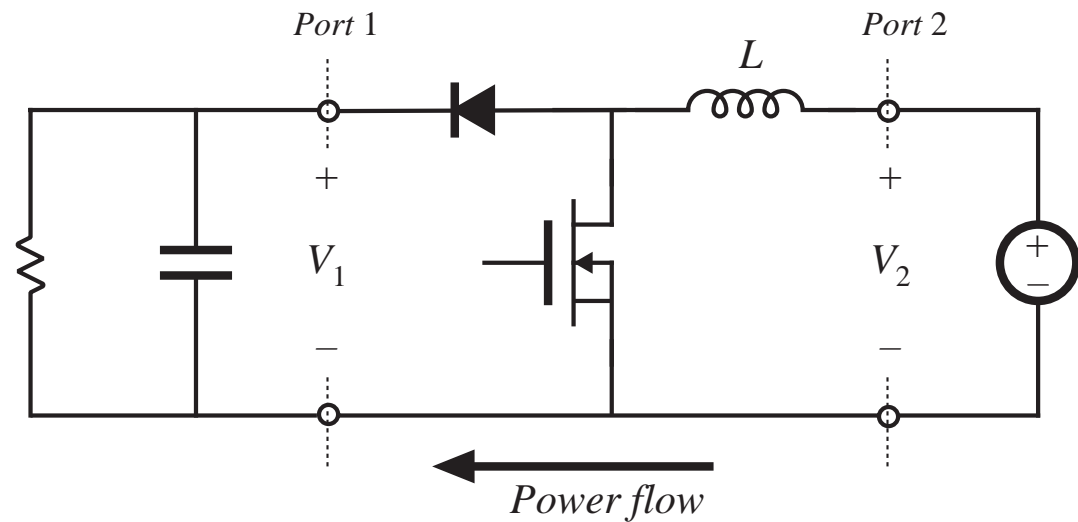
# Realization of switches as in Chapter 4


- Reversal of power flow requires new realization of switches
- Transistor conducts when switch is in position 2
- Interchange of  $D$  and  $D'$



$$V_1 = \frac{1}{D'} V_2$$


Inversion of buck converter yields boost converter
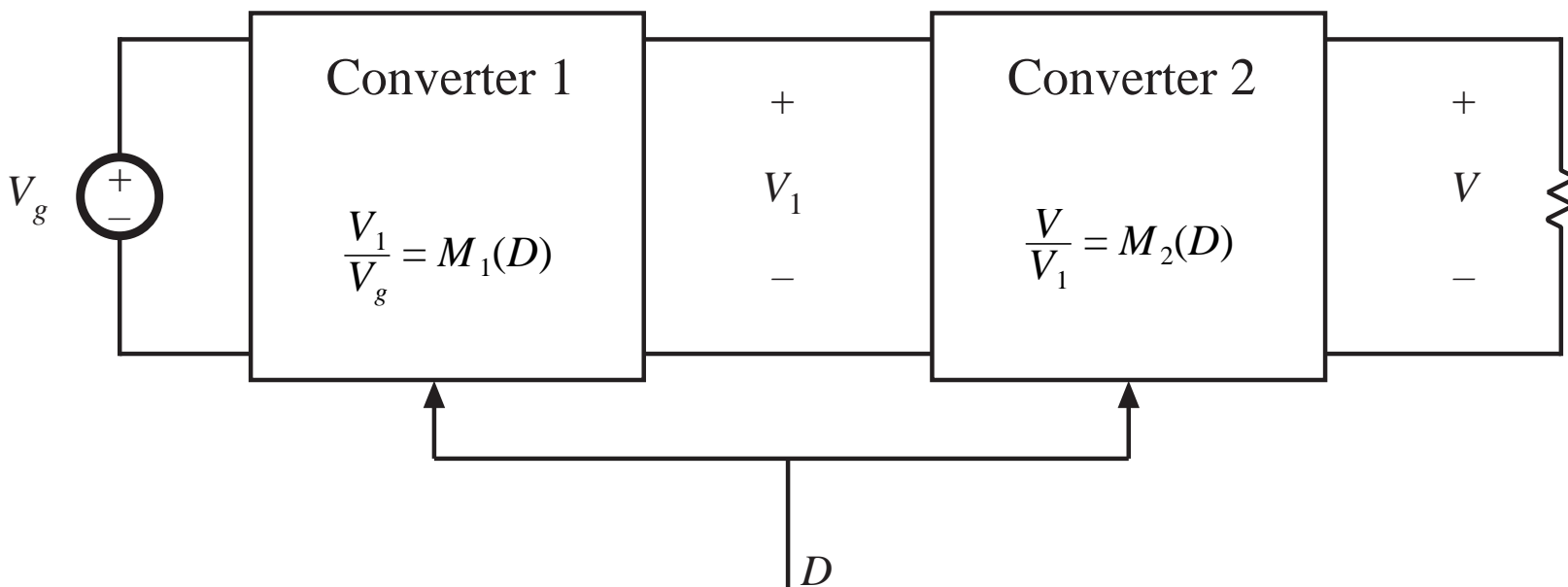
## 6.1.2. Cascade connection of converters



$$\begin{aligned} V_1 &= M_1(D) V_g \\ V &= M_2(D) V_1 \end{aligned} \quad \longrightarrow \quad \frac{V}{V_g} = M(D) = M_1(D) M_2(D)$$


## Example: buck cascaded by boost

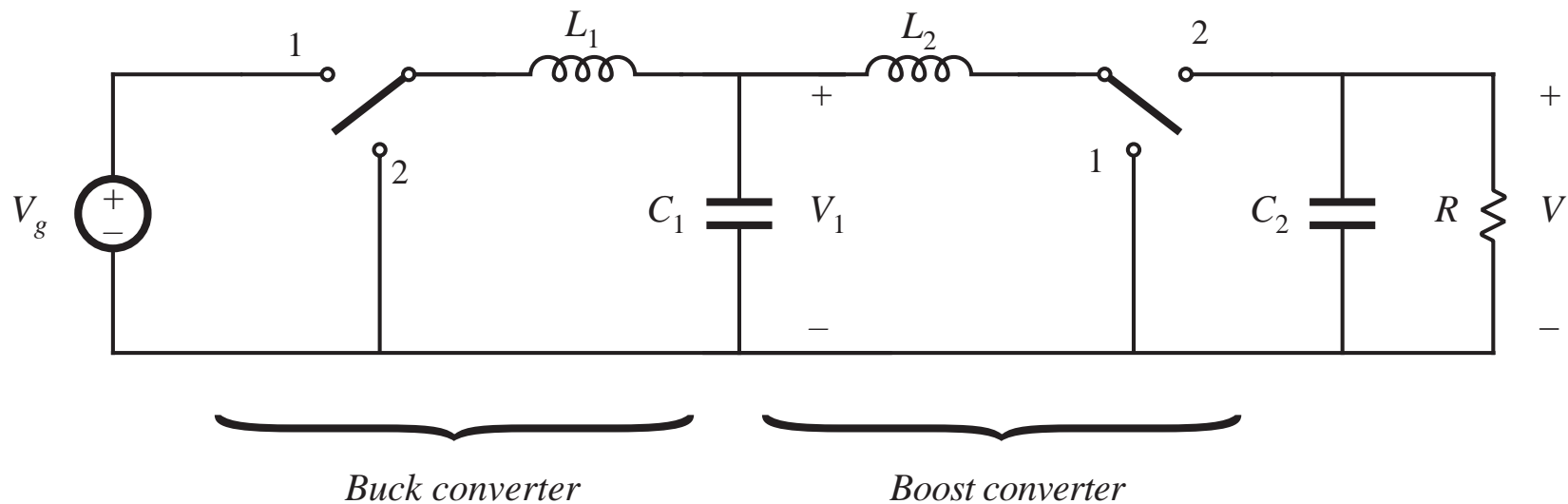


$$\frac{V_1}{V_g} = D$$
$$\frac{V}{V_1} = \frac{1}{1-D}$$
$$\frac{V}{V_g} = \frac{D}{1-D}$$

# Buck cascaded by boost: simplification of internal filter


Remove capacitor  $C_1$

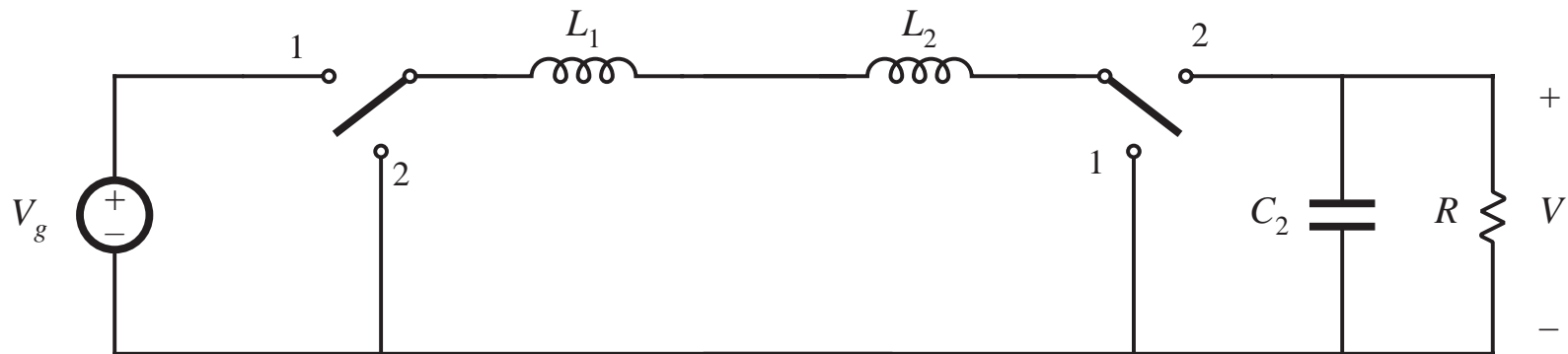

Combine inductors  $L_1$  and  $L_2$


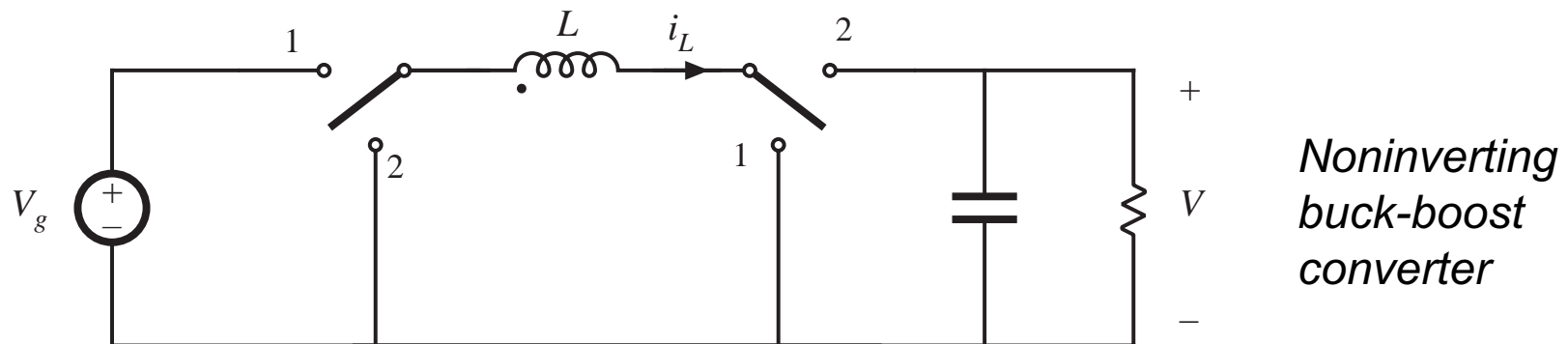


# Noninverting buck-boost converter

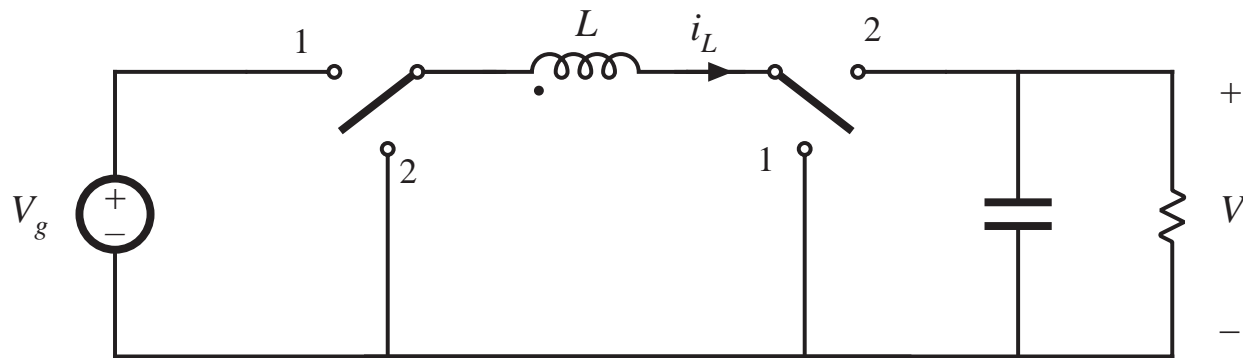


*subinterval 1*

*subinterval 2*

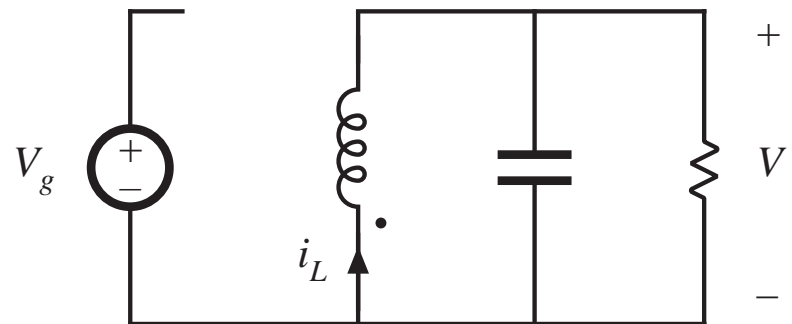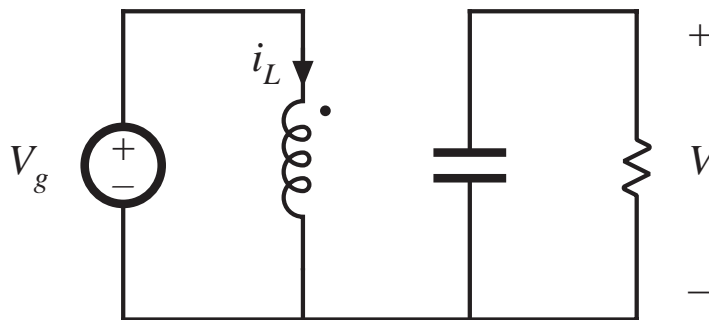




# Reversal of output voltage polarity

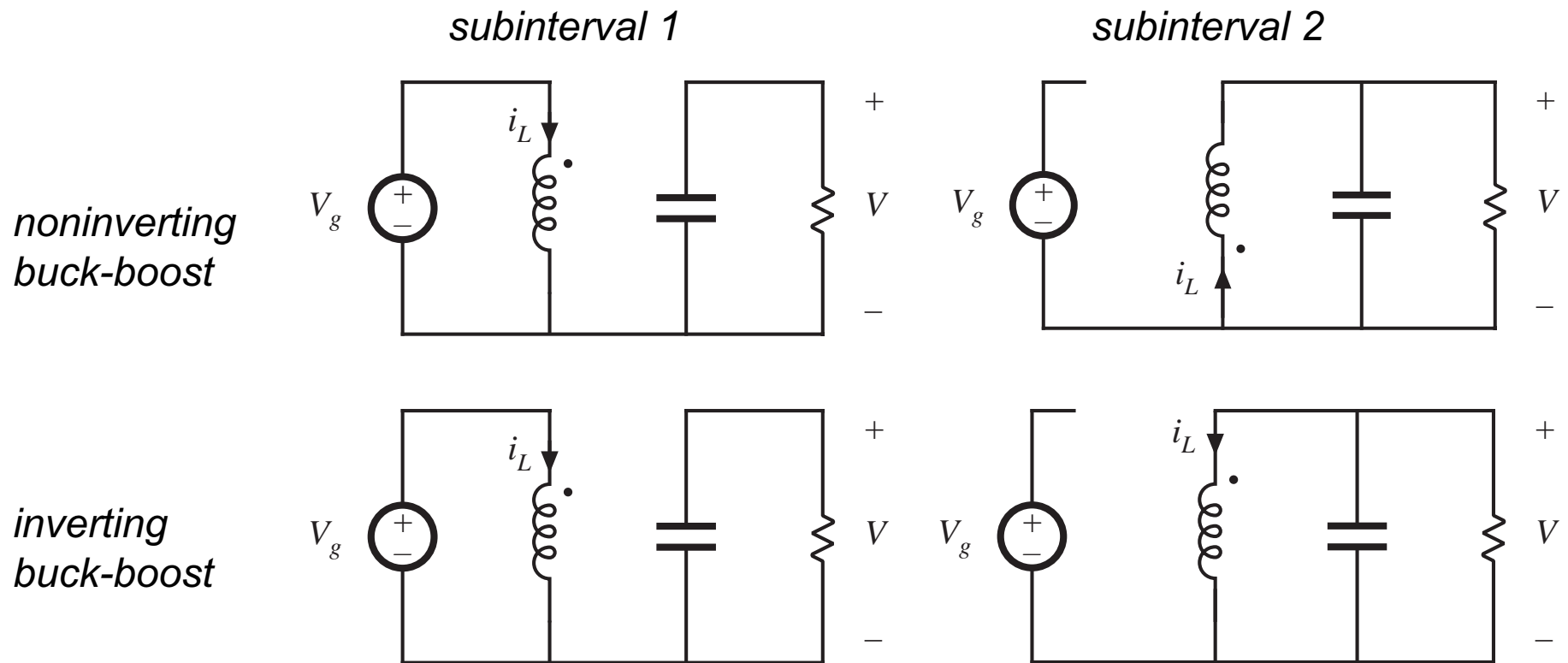


# Reduction of number of switches: inverting buck-boost


*Subinterval 1*

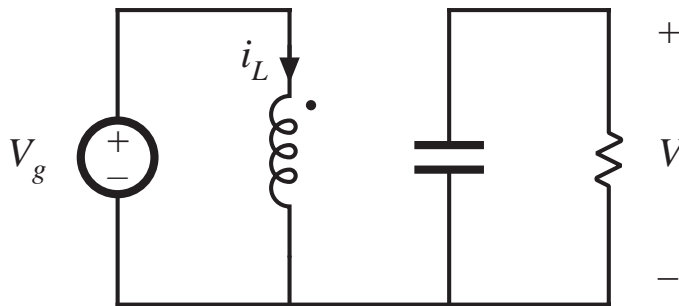

*Subinterval 2*

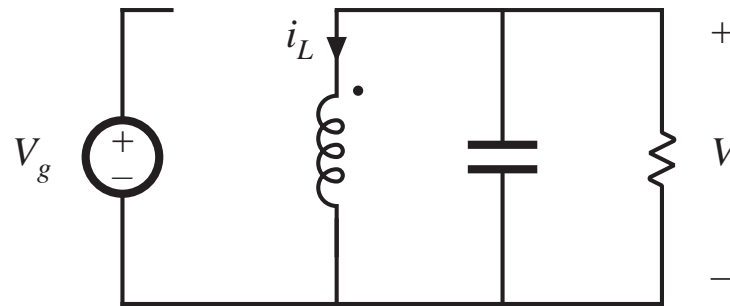

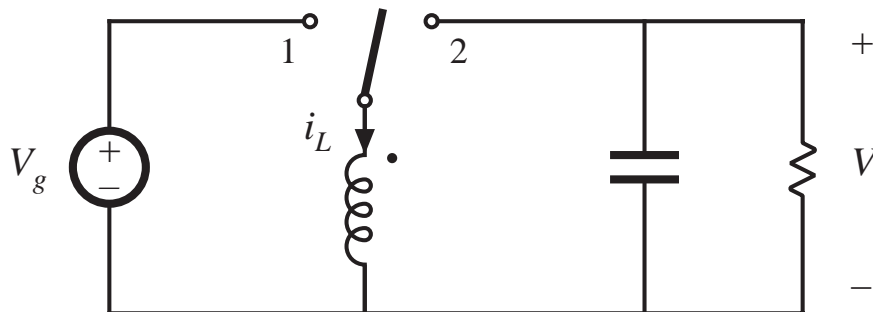One side of inductor always connected to ground  
— hence, only one SPDT switch needed:



$$\frac{V}{V_g} = -\frac{D}{1-D}$$

# Discussion: cascade connections

---

- Properties of buck-boost converter follow from its derivation as buck cascaded by boost

Equivalent circuit model: buck  $1:D$  transformer cascaded by boost  $D':1$  transformer

Pulsating input current of buck converter

Pulsating output current of boost converter

- Other cascade connections are possible

Cuk converter: boost cascaded by buck