7.3 State Space Averaging

- A formal method for deriving the small-signal ac equations of a switching converter
- Equivalent to the modeling method of the previous sections
- Uses the state-space matrix description of linear circuits
- Often cited in the literature
- A general approach: if the state equations of the converter can be written for each subinterval, then the small-signal averaged model can always be derived
- Computer programs exist which utilize the state-space averaging method

7.3.1 The state equations of a network

- A canonical form for writing the differential equations of a system
- If the system is linear, then the derivatives of the *state variables* are expressed as linear combinations of the system independent inputs and state variables themselves
- The physical state variables of a system are usually associated with the storage of energy
- For a typical converter circuit, the physical state variables are the inductor currents and capacitor voltages
- Other typical physical state variables: position and velocity of a motor shaft
- At a given point in time, the values of the state variables depend on the previous history of the system, rather than the present values of the system inputs
- To solve the differential equations of a system, the initial values of the state variables must be specified

Fundamentals of Power Electronics 66 *Chapter 7: AC equivalent circuit modeling*

State equations of a linear system, in matrix form

Input vector $\mathbf{u}(t)$ contains independent sources such as $v_g(t)$

Output vector **y**(*t*) contains other dependent quantities to be computed, such as $i_g(t)$

Matrix **K** contains values of capacitance, inductance, and mutual inductance, so that **K** d**x**/d*t* is a vector containing capacitor currents and inductor winding voltages. These quantities are expressed as linear combinations of the independent inputs and state variables. The matrices **A**, **B**, **C**, and **E** contain the constants of proportionality.

Example

To write the state equations of this circuit, we must express the inductor voltages and capacitor currents as linear combinations of the elements of the $\mathbf{x}(t)$ and $\mathbf{u}(t)$ vectors.

Fundamentals of Power Electronics 68 *Chapter 7: AC equivalent circuit modeling*

Circuit equations

Fundamentals of Power Electronics 69 *Chapter 7: AC equivalent circuit modeling*

Equations in matrix form

The same equations:

$$
i_{C1}(t) = C_1 \frac{dv_1(t)}{dt} = i_{in}(t) - \frac{v_1(t)}{R} - i(t)
$$

$$
i_{C2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}
$$

$$
v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)
$$

Express in matrix form:

$$
\begin{bmatrix}\nC_1 & 0 & 0 \\
0 & C_2 & 0 \\
0 & 0 & L\n\end{bmatrix}\n\begin{bmatrix}\n\frac{dv_1(t)}{dt} \\
\frac{dv_2(t)}{dt} \\
\frac{di(t)}{dt}\n\end{bmatrix} =\n\begin{bmatrix}\n-\frac{1}{R_1} & 0 & -1 \\
0 & -\frac{1}{R_2 + R_3} & 1 \\
1 & -1 & 0\n\end{bmatrix}\n\begin{bmatrix}\nv_1(t) \\
v_2(t) \\
i(t)\n\end{bmatrix} +\n\begin{bmatrix}\n1 \\
0 \\
0\n\end{bmatrix}\n\begin{bmatrix}\ni_{in}(t) \\
i_{in}(t)\n\end{bmatrix}
$$
\n**K**\n
$$
\frac{d\mathbf{x}(t)}{dt} = \mathbf{A} \qquad \mathbf{x}(t) + \mathbf{B} \quad \mathbf{u}(t)
$$

Fundamentals of Power Electronics 70 *Chapter 7: AC equivalent circuit modeling*

Output (dependent signal) equations

Express elements of the vector **y** as linear combinations of elements of **x** and **u**:

$$
v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}
$$

$$
i_{R1}(t) = \frac{v_1(t)}{R_1}
$$

Fundamentals of Power Electronics 71 *Chapter 7: AC equivalent circuit modeling*

Express in matrix form

The same equations: $v_{out}(t) = v_2(t) \frac{R_3}{R_3}$ $R_2 + R_3$ $i_{R1}(t) =$ $v_1(t)$ R_{1}

Express in matrix form:

$$
\underbrace{\begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 0 & \frac{R_3}{R_2 + R_3} & 0 \\ \frac{1}{R_1} & 0 & 0 \end{bmatrix}}_{\mathbf{C}} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{y}(t)} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{y}(t)}
$$
\n
$$
\mathbf{y}(t) = \underbrace{\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}}_{\mathbf{x}(t)} + \mathbf{E} \mathbf{u}(t)
$$

7.3.2 The basic state-space averaged model

Given: a PWM converter, operating in continuous conduction mode, with two subintervals during each switching period.

During subinterval 1*,* when the switches are in position 1, the converter reduces to a linear circuit that can be described by the following state equations:

$$
\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)
$$

$$
\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)
$$

During subinterval 2*,* when the switches are in position 2, the converter reduces to another linear circuit, that can be described by the following state equations:

$$
\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_2 \mathbf{x}(t) + \mathbf{B}_2 \mathbf{u}(t)
$$

$$
\mathbf{y}(t) = \mathbf{C}_2 \mathbf{x}(t) + \mathbf{E}_2 \mathbf{u}(t)
$$

Fundamentals of Power Electronics 73 *Chapter 7: AC equivalent circuit modeling*

Equilibrium (dc) state-space averaged model

Provided that the natural frequencies of the converter, as well as the frequencies of variations of the converter inputs, are much slower than the switching frequency, then the state-space averaged model that describes the converter in equilibrium is

$$
0 = A X + B U
$$

$$
Y = C X + E U
$$

Solution of equilibrium averaged model

Equilibrium state-space averaged model:

 $0 = A X + B U$ $Y = C X + E U$

Solution for **X** and **Y**:

 $X = -A^{-1}BU$ $\mathbf{Y} = \left(-\mathbf{C} \mathbf{A}^{-1} \mathbf{B} + \mathbf{E}\right) \mathbf{U}$

Small-signal ac state-space averaged model

$$
\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A}\ \hat{\mathbf{x}}(t) + \mathbf{B}\ \hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{A}_1 - \mathbf{A}_2 \right) \mathbf{X} + \left(\mathbf{B}_1 - \mathbf{B}_2 \right) \mathbf{U} \right\} \hat{d}(t)
$$

$$
\hat{\mathbf{y}}(t) = \mathbf{C}\ \hat{\mathbf{x}}(t) + \mathbf{E}\ \hat{\mathbf{u}}(t) + \left\{ \left(\mathbf{C}_1 - \mathbf{C}_2 \right) \mathbf{X} + \left(\mathbf{E}_1 - \mathbf{E}_2 \right) \mathbf{U} \right\} \hat{d}(t)
$$

where

x(*t*) = *small* – *signal* (*ac*) *perturbation in state vector* $\hat{\mathbf{u}}(t) = \text{small} - \text{signal}(ac)$ perturbation in input vector **y**(*t*) = *small* – *signal* (*ac*) *perturbation in output vector* $\hat{d}(t) = \text{small} - \text{signal}(ac)$ perturbation in duty cycle

So if we can write the converter state equations during subintervals 1 and 2, then we can always find the averaged dc and small-signal ac models

7.3.3 Discussion of the state-space averaging result

As in Sections 7.1 and 7.2, the low-frequency components of the inductor currents and capacitor voltages are modeled by averaging over an interval of length T_s . Hence, we define the average of the state vector as:

$$
\langle \mathbf{x}(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} \mathbf{x}(\tau) d\tau
$$

The low-frequency components of the input and output vectors are modeled in a similar manner.

By averaging the inductor voltages and capacitor currents, one obtains:

$$
\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}
$$

Fundamentals of Power Electronics 77 *Chapter 7: AC equivalent circuit modeling*

Change in state vector during first subinterval

During subinterval 1, we have

$$
\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t)
$$

$$
\mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t)
$$

So the elements of **x**(*t*) change with the slope

$$
\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1}\left(\mathbf{A}_1\mathbf{x}(t) + \mathbf{B}_1\mathbf{u}(t)\right)
$$

Small ripple assumption: the elements of $x(t)$ and $u(t)$ do not change significantly during the subinterval. Hence the slopes are essentially constant and are equal to

$$
\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)
$$

Fundamentals of Power Electronics 78 *Chapter 7: AC equivalent circuit modeling*

Change in state vector during first subinterval

Fundamentals of Power Electronics 79 *Chapter 7: AC equivalent circuit modeling*

Change in state vector during second subinterval

Use similar arguments.

State vector now changes with the essentially constant slope

$$
\frac{d\mathbf{x}(t)}{dt} = \mathbf{K}^{-1} \left(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)
$$

The value of the state vector at the end of the second subinterval is therefore

$$
\underbrace{\mathbf{x}(T_s)}_{\text{final}} = \underbrace{\mathbf{x}(dT_s)}_{\text{initial}} + \underbrace{(d^T r_s)}_{\text{interval}} \underbrace{\mathbf{K}^{-1} \left(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s}}_{\text{slope}}
$$
\nvalue value value length

Fundamentals of Power Electronics 80 *Chapter 7: AC equivalent circuit modeling*

Net change in state vector over one switching period

We have:

$$
\mathbf{x}(dT_s) = \mathbf{x}(0) + \left(dT_s \right) \mathbf{K}^{-1} \left(\mathbf{A}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)
$$

$$
\mathbf{x}(T_s) = \mathbf{x}(dT_s) + \left(d^{\prime} T_s \right) \mathbf{K}^{-1} \left(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)
$$

Eliminate $\mathbf{x}(dT_s)$, to express $\mathbf{x}(T_s)$ directly in terms of $\mathbf{x}(0)$:

$$
\mathbf{x}(T_s) = \mathbf{x}(0) + dT_s \mathbf{K}^{-1} \Big(\mathbf{A}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \Big) + d^T T_s \mathbf{K}^{-1} \Big(\mathbf{A}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{B}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \Big)
$$

Collect terms:

$$
\mathbf{x}(T_s) = \mathbf{x}(0) + T_s \mathbf{K}^{-1} \Big(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \Big) \Big\langle \mathbf{x}(t) \Big\rangle_{T_s} + T_s \mathbf{K}^{-1} \Big(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \Big) \Big\langle \mathbf{u}(t) \Big\rangle_{T_s}
$$

Fundamentals of Power Electronics 81 *Chapter 7: AC equivalent circuit modeling*

Approximate derivative of state vector

Use Euler approximation:

$$
\frac{d\left\langle \mathbf{x}(t)\right\rangle_{T_s}}{dt} \approx \frac{\mathbf{x}(T_s) - \mathbf{x}(0)}{T_s}
$$

We obtain:

$$
\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}
$$

Fundamentals of Power Electronics 82 *Chapter 7: AC equivalent circuit modeling*

Low-frequency components of output vector

Remove switching harmonics by averaging over one switching period:

$$
\left\langle \mathbf{y}(t) \right\rangle_{T_s} = d(t) \left(\mathbf{C}_1 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{E}_1 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right) + d'(t) \left(\mathbf{C}_2 \left\langle \mathbf{x}(t) \right\rangle_{T_s} + \mathbf{E}_2 \left\langle \mathbf{u}(t) \right\rangle_{T_s} \right)
$$

Collect terms:

$$
\langle \mathbf{y}(t) \rangle_{T_s} = \left(d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}
$$

Fundamentals of Power Electronics 83 *Chapter 7: AC equivalent circuit modeling*

Averaged state equations: quiescent operating point

The averaged (nonlinear) state equations:

$$
\mathbf{K} \frac{d\langle \mathbf{x}(t) \rangle_{T_s}}{dt} = \left(d(t) \mathbf{A}_1 + d'(t) \mathbf{A}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{B}_1 + d'(t) \mathbf{B}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}
$$

$$
\langle \mathbf{y}(t) \rangle_{T_s} = \left(d(t) \mathbf{C}_1 + d'(t) \mathbf{C}_2 \right) \langle \mathbf{x}(t) \rangle_{T_s} + \left(d(t) \mathbf{E}_1 + d'(t) \mathbf{E}_2 \right) \langle \mathbf{u}(t) \rangle_{T_s}
$$

The converter operates in equilibrium when the derivatives of all elements of $\langle x(t) \rangle_{T_s}$ are zero. Hence, the converter quiescent operating point is the solution of

$$
0 = A X + B U
$$

$$
Y = C X + E U
$$

where $A = D A_1 + D' A_2$ $\mathbf{B} = D \mathbf{B}_1 + D' \mathbf{B}_2$ $\mathbf{E} = D \mathbf{E}_1 + D' \mathbf{E}_2$ and

 $\mathbf{C} = D \mathbf{C}_1 + D' \mathbf{C}_2$ $\mathbf{Y} = equilibrium \ (dc) \ output \ vector$ **X** = *equilibrium* (*dc*) *state vector* **U** = *equilibrium* (*dc*) *input vector D* = *equilibrium* (*dc*) *duty cycle*

Fundamentals of Power Electronics 84 *Chapter 7: AC equivalent circuit modeling*

Averaged state equations: perturbation and linearization

Substitute into averaged state equations:

$$
\mathbf{K} \frac{d(\mathbf{X} + \hat{\mathbf{x}}(t))}{dt} = \left(\left(D + \hat{d}(t) \right) \mathbf{A}_1 + \left(D' - \hat{d}(t) \right) \mathbf{A}_2 \right) \left(\mathbf{X} + \hat{\mathbf{x}}(t) \right)
$$

$$
+ \left(\left(D + \hat{d}(t) \right) \mathbf{B}_1 + \left(D' - \hat{d}(t) \right) \mathbf{B}_2 \right) \left(\mathbf{U} + \hat{\mathbf{u}}(t) \right)
$$

$$
\left(\mathbf{Y} + \hat{\mathbf{y}}(t) \right) = \left(\left(D + \hat{d}(t) \right) \mathbf{C}_1 + \left(D' - \hat{d}(t) \right) \mathbf{C}_2 \right) \left(\mathbf{X} + \hat{\mathbf{x}}(t) \right)
$$

$$
+ \left(\left(D + \hat{d}(t) \right) \mathbf{E}_1 + \left(D' - \hat{d}(t) \right) \mathbf{E}_2 \right) \left(\mathbf{U} + \hat{\mathbf{u}}(t) \right)
$$

Fundamentals of Power Electronics 85 *Chapter 7: AC equivalent circuit modeling*

Averaged state equations: perturbation and linearization

Linearized small-signal state equations

Dc terms drop out of equations. Second-order (nonlinear) terms are small when the small-signal assumption is satisfied. We are left with:

$$
\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A}\hat{\mathbf{x}}(t) + \mathbf{B}\hat{\mathbf{u}}(t) + \left\{ (\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U} \right\} \hat{d}(t)
$$

$$
\hat{\mathbf{y}}(t) = \mathbf{C}\hat{\mathbf{x}}(t) + \mathbf{E}\hat{\mathbf{u}}(t) + \left\{ (\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U} \right\} \hat{d}(t)
$$

This is the desired result.