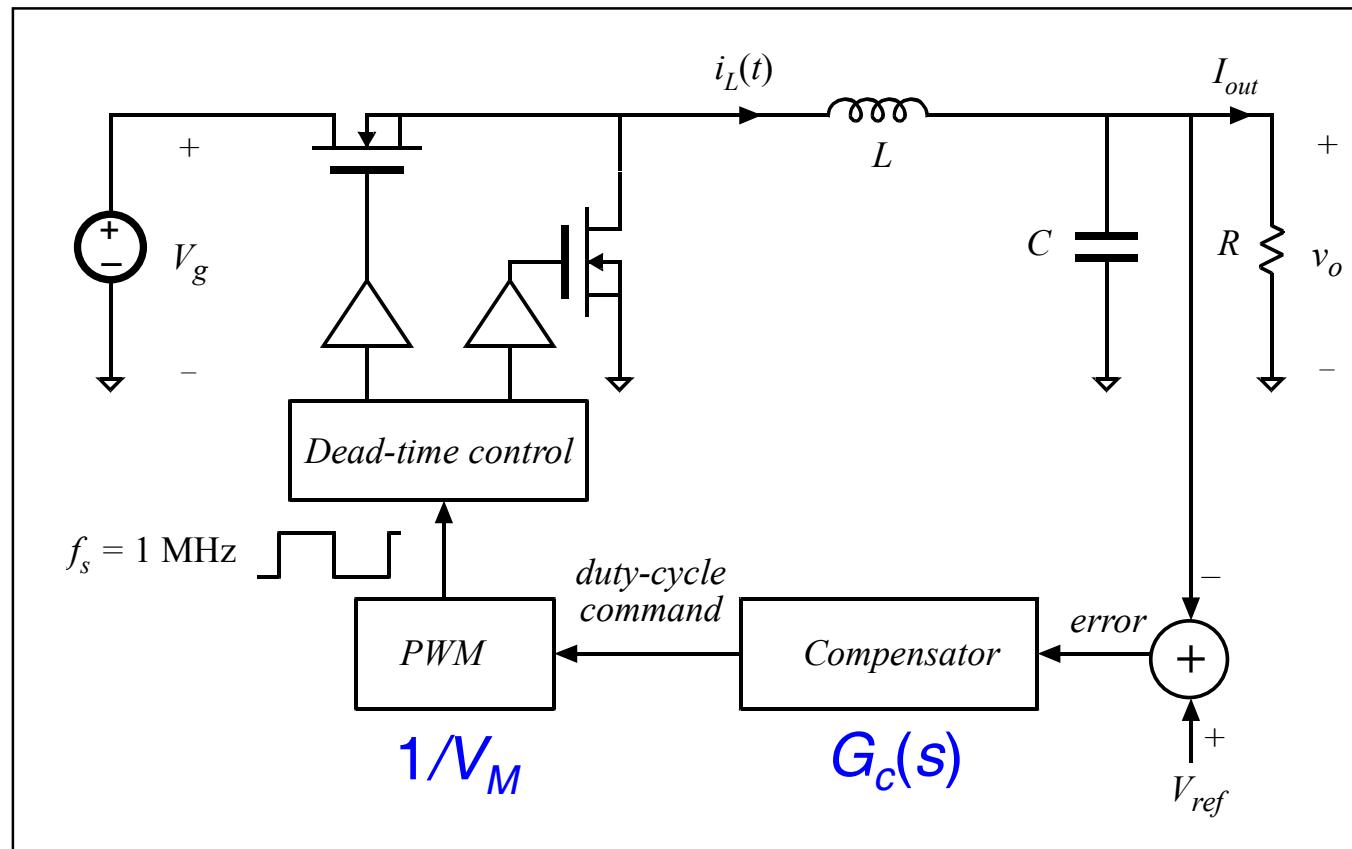


Another Compensator Design Example




Point-of-Load Synchronous Buck Regulator

Power stage parameters

- Switching frequency:
 $f_s = 1 \text{ MHz}$
- $V_{ref} = 1.8 \text{ V}$
- $I_{out} = 0 \text{ to } 5 \text{ A}$
- $V_g = 5 \text{ V}$
- $L = 1 \mu\text{H}$
- $R_L = 30 \text{ m}\Omega$
- $C = 200 \mu\text{F}$
- $R_{esr} = 0.8 \text{ m}\Omega$
- $V_M = 1 \text{ V}$
- $H = 1$

Buck Averaged Small-Signal Model

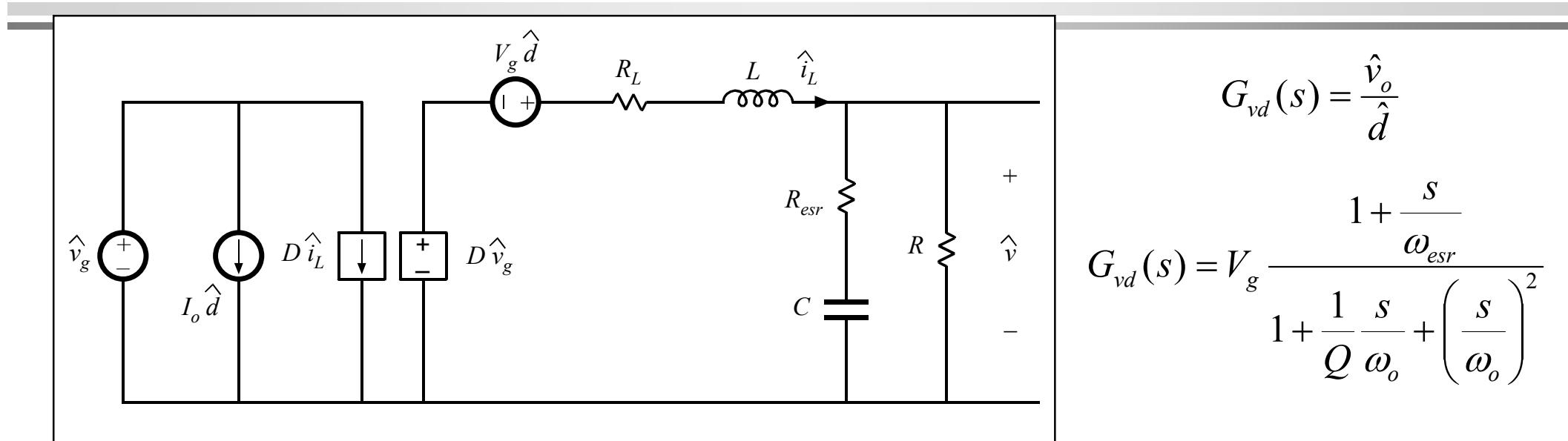

$$G_{vd}(s) = \frac{\hat{v}_o}{\hat{d}}$$

$$G_{vd}(s) = V_g \frac{1 + \frac{s}{\omega_{esr}}}{1 + \frac{1}{Q} \frac{s}{\omega_o} + \left(\frac{s}{\omega_o}\right)^2}$$

Pair of poles:

$$f_o = \frac{1}{2\pi\sqrt{CL}} = 11 \text{ kHz}$$

$$Q_{loss} = \frac{\sqrt{L/C}}{R_{esr} + R_L} = 2.3 \rightarrow 7.2 \text{ dB} \quad Q_{load} = \frac{R}{\sqrt{L/C}} > 5$$

$$Q = Q_{loss} \parallel Q_{load} = \frac{Q_{loss}Q_{load}}{Q_{loss} + Q_{load}} < 2.3 \rightarrow 7.2 \text{ dB}$$


Low-frequency gain
(including PWM gain):

$$G_{vdo} \frac{1}{V_M} = 5 \rightarrow 14 \text{ dB}$$

ESR zero:

$$f_{esr} = \frac{1}{2\pi CR_{esr}} = 1 \text{ MHz}$$


Uncompensated loop gain T_u

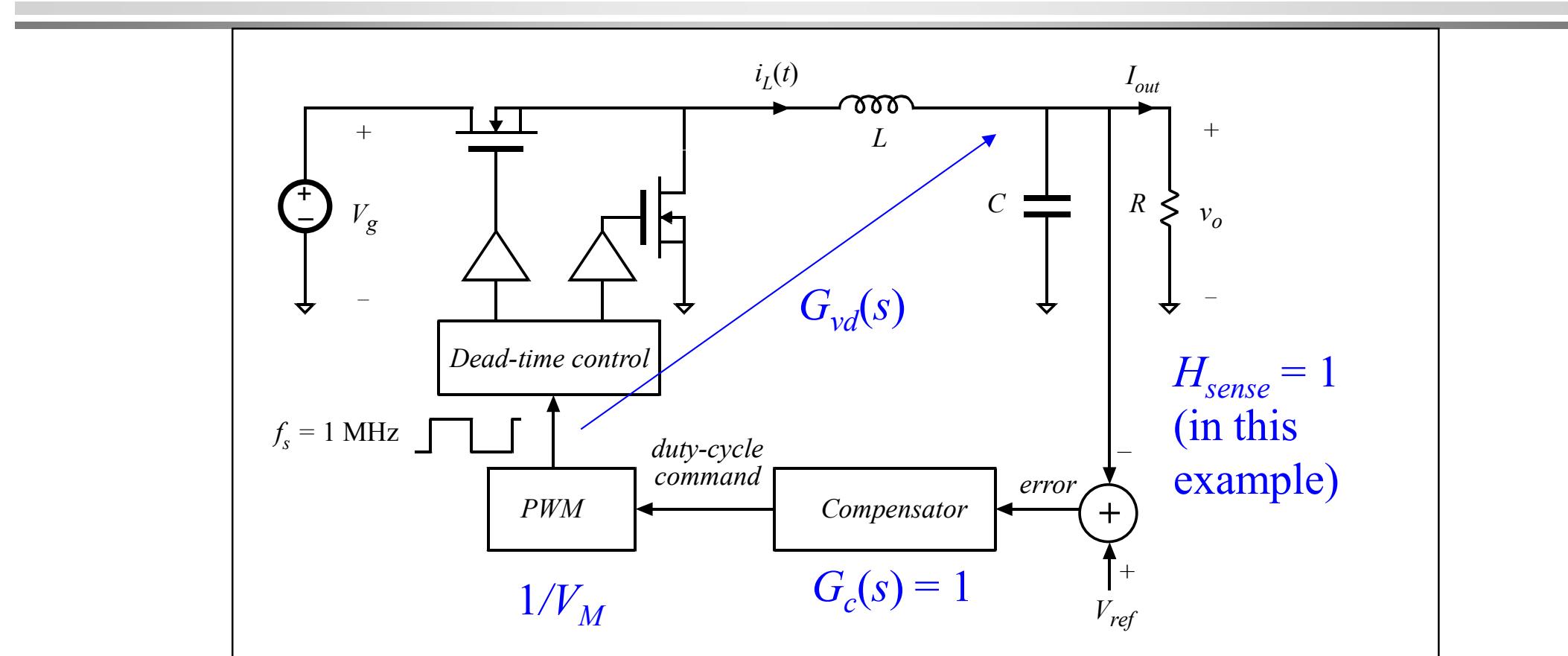


$$T_u(s) = H_{sense}(1/V_M)G_{vd}(s)$$

Plot magnitude and phase responses of $T_u(s)$ to plan how to design $G_c(s)$

Magnitude and phase Bode plots of T_u

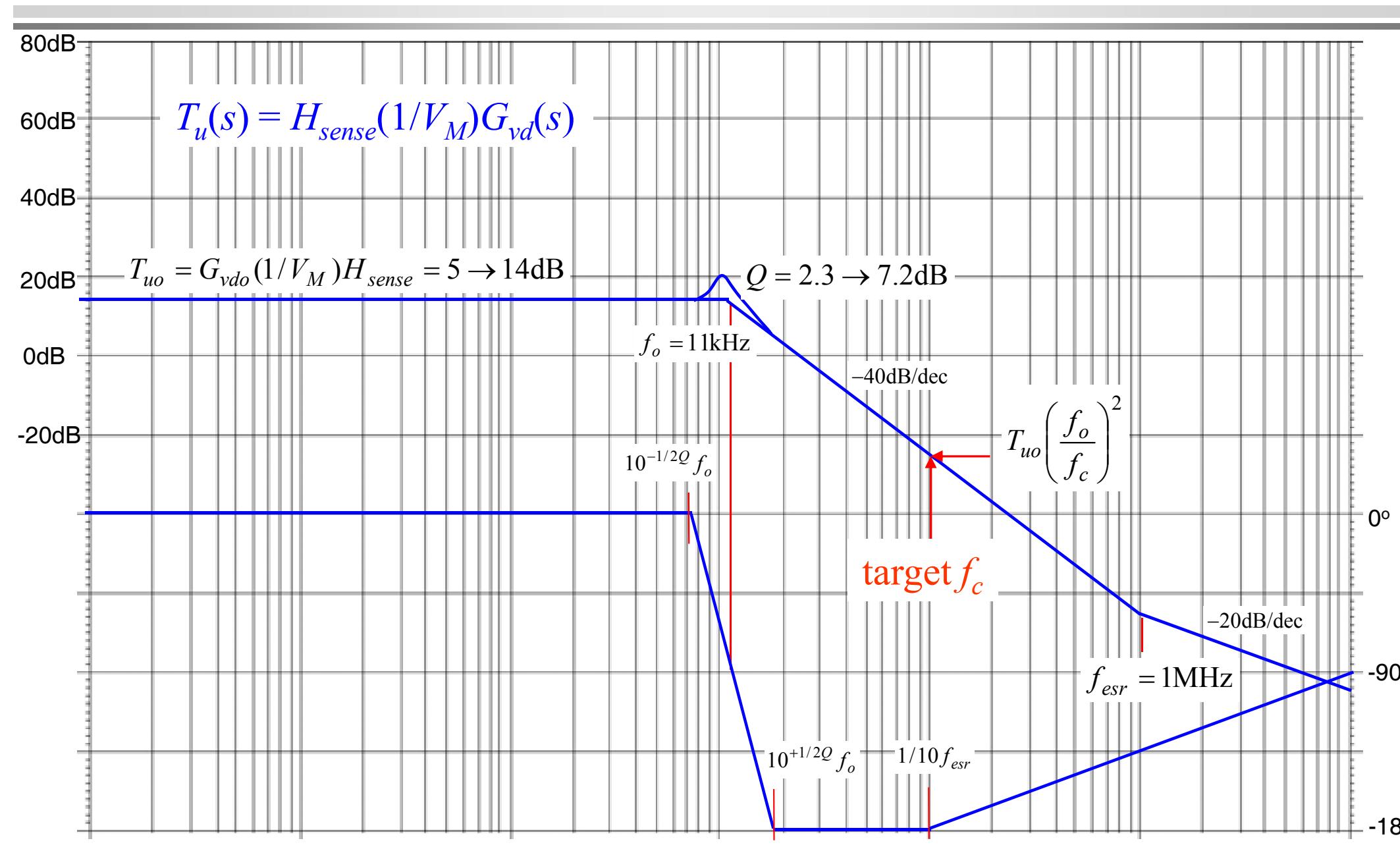


Magnitude and phase Bode plots of T_u

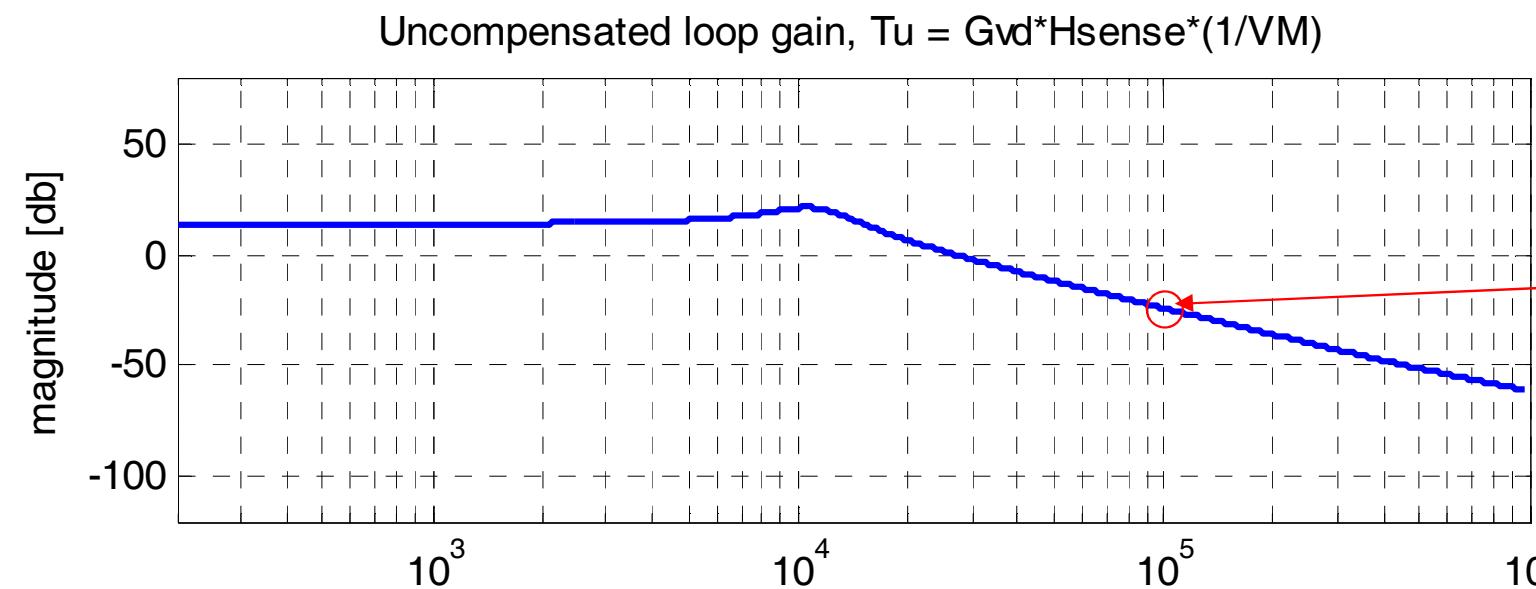

Exact magnitude and phase responses (MATLAB)

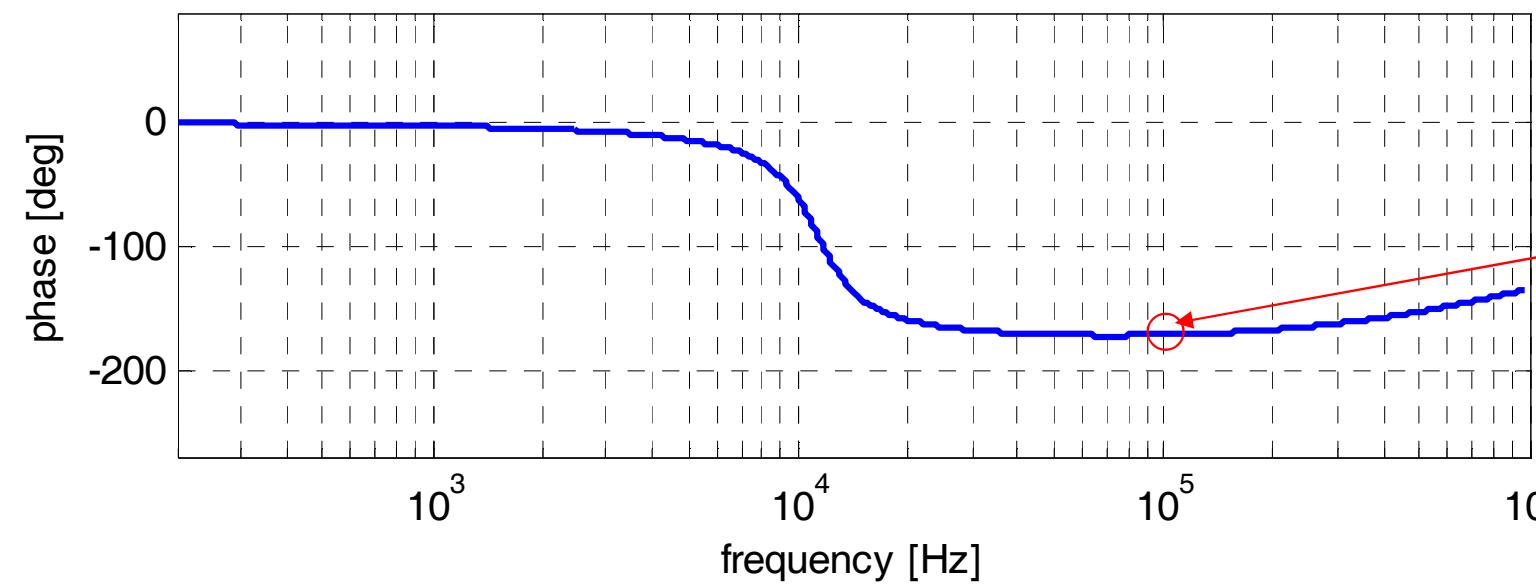Target cross-over frequency
 $f_c = f_s/10 = 100 \text{ kHz}$



No phase margin:
a lead (PD)
compensator is
required

Lead (PD) compensator design

1. Choose: $f_c = 100 \text{ kHz}$

$$\theta = \varphi_m = 53^\circ$$

2. Compute:

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}} = 33 \text{ kHz}$$


$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}} = 300 \text{ kHz}$$

3. Find G_{co} to position the crossover frequency:

$$T_{uo} \left(\frac{f_o}{f_c} \right)^2 G_{co} \sqrt{\frac{f_p}{f_z}} = 1 \quad \rightarrow \quad G_{co} = \frac{1}{T_{uo}} \left(\frac{f_c}{f_o} \right)^2 \sqrt{\frac{f_z}{f_p}} = 5.45 \rightarrow 15 \text{ dB}$$

$\underbrace{}$ $\underbrace{}$

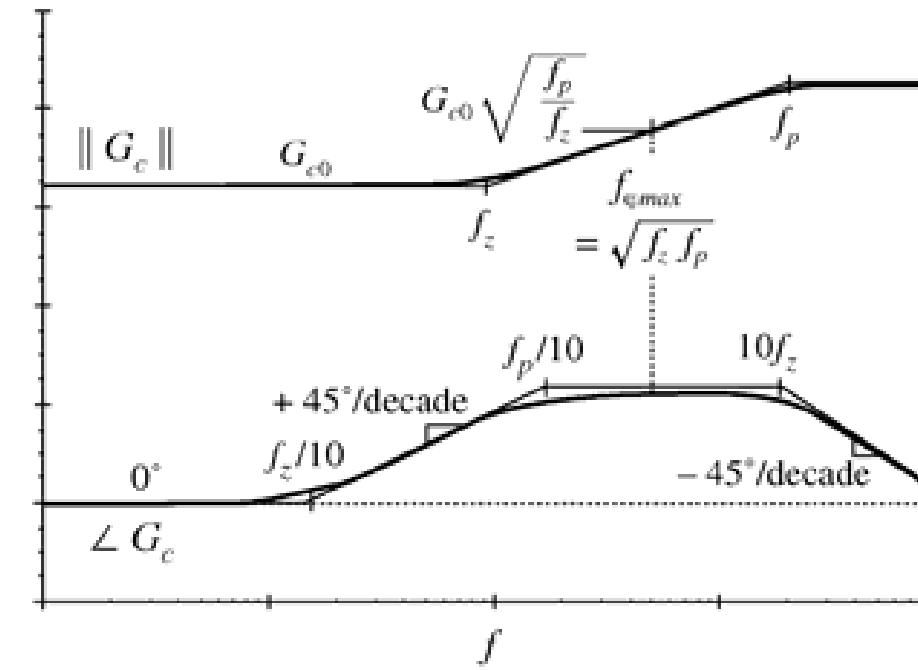Magnitude of T_u at f_c Magnitude of G_c at f_c



Lead (PD) compensator summary

$$G_c(s) = G_{co} \frac{\left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}$$

Lead
compensator HF pole


$G_{co} = 5.45 \rightarrow 15 \text{ dB}$
 $f_z = 33 \text{ kHz}$
 $f_{p1} = 300 \text{ kHz}$
 $f_c = 100 \text{ kHz} \quad (=1/10 \text{ of } f_s)$

High-frequency gain of the lead compensator: $G_{co}f_{p1}/f_z = 49$ (34 dB)

Added high-frequency pole: $f_{p2} = 1 \text{ MHz}$ ($=f_{esr} = f_s$ in this example)

Practical implementation would require an op-amp with a gain bandwidth product of at least $49*f_{p2} = 49 \text{ MHz}$


Loop gain with lead (PD) compensator

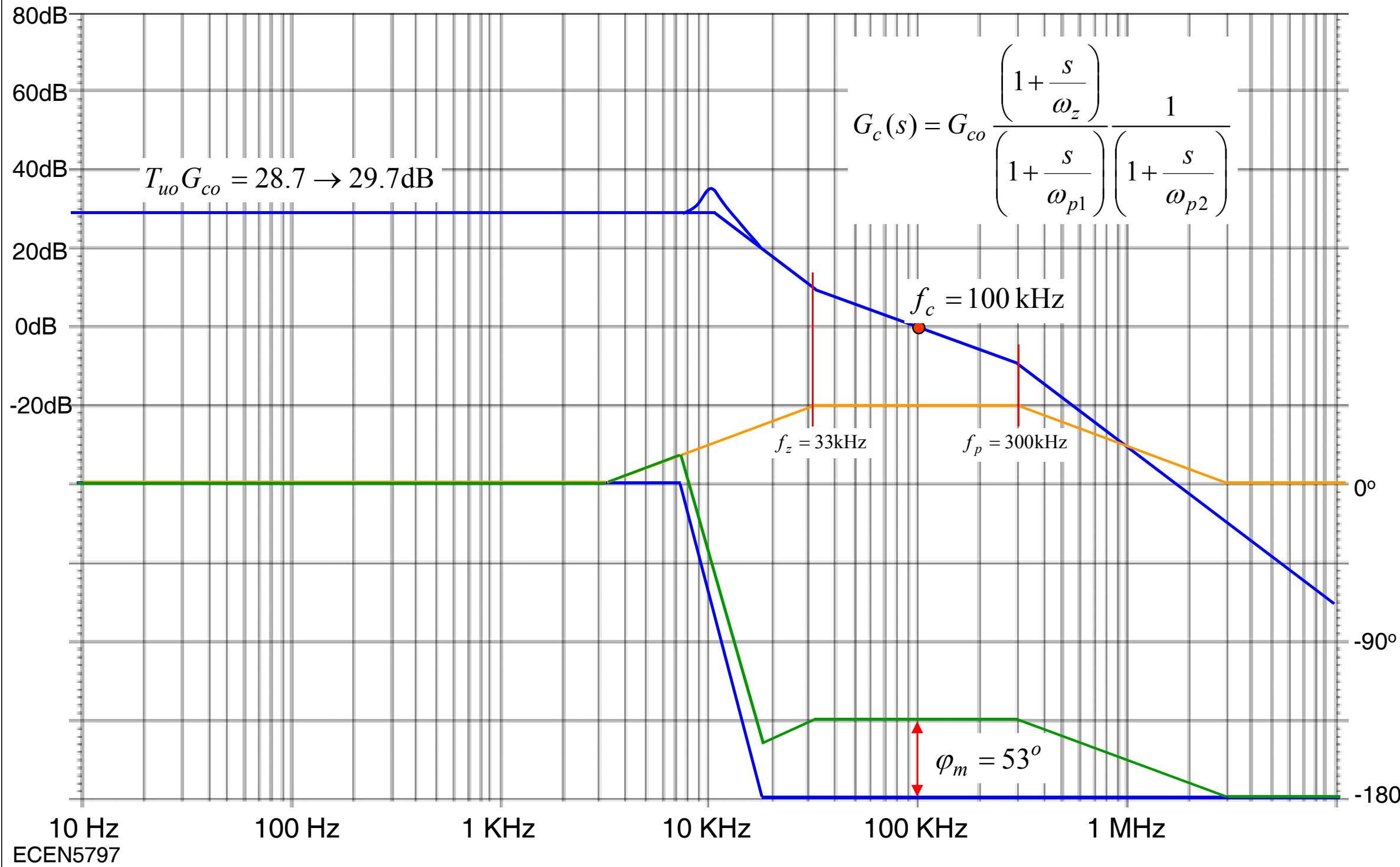

Add lag (PI) compensator

$$G_c(s) = G_{c\infty} \left(1 + \frac{\omega_L}{s} \right)$$

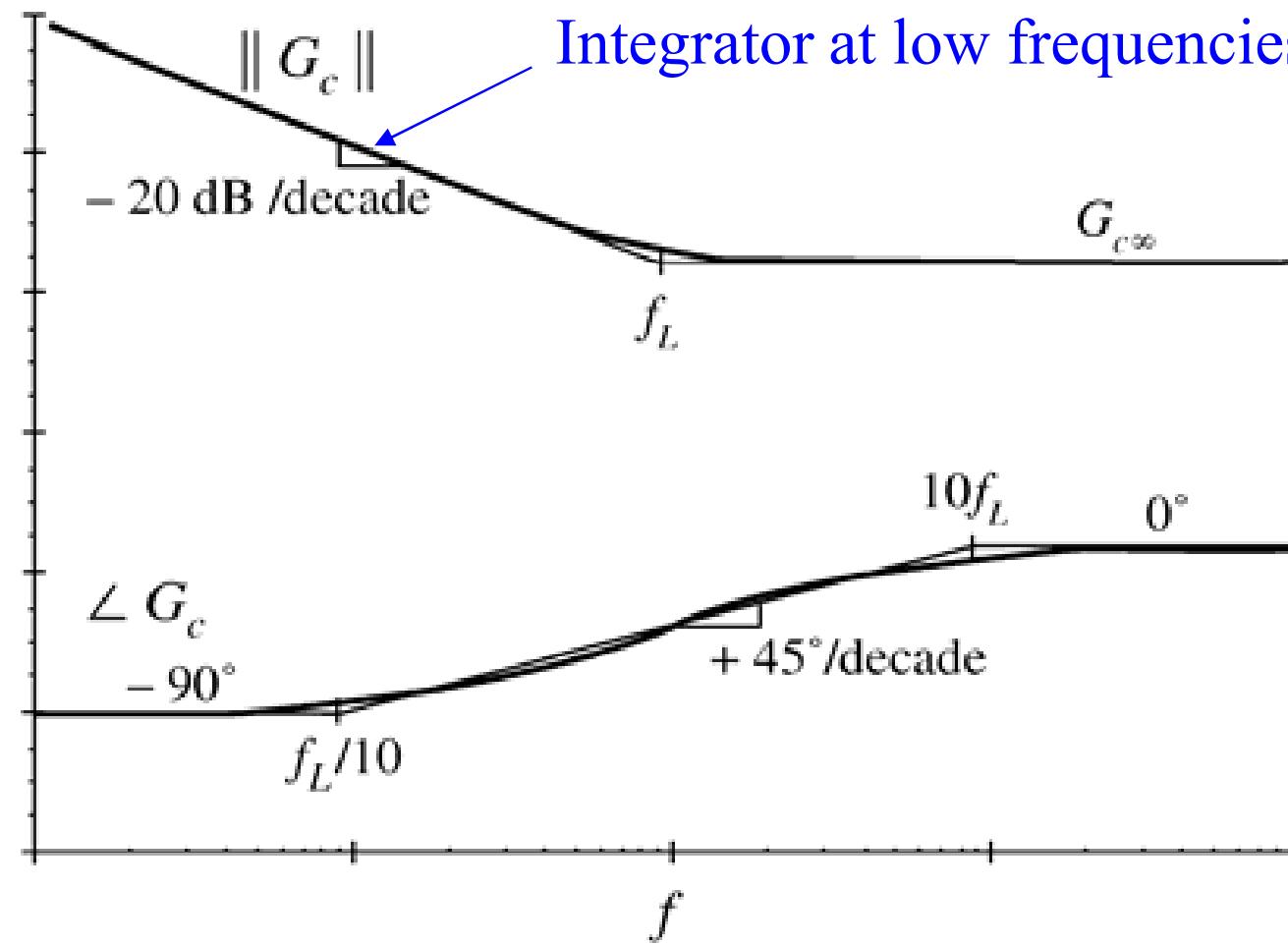
Improves low-frequency loop gain and regulation




Choose $10f_L < f_c$ so that phase margin stays approximately the same: $f_L = 8 \text{ kHz}$

Keep the same cross-over frequency: $G_{c\infty} = G_{co} = G_{cm} = 5.45 \rightarrow 15 \text{ dB}$

Adding PI Compensator

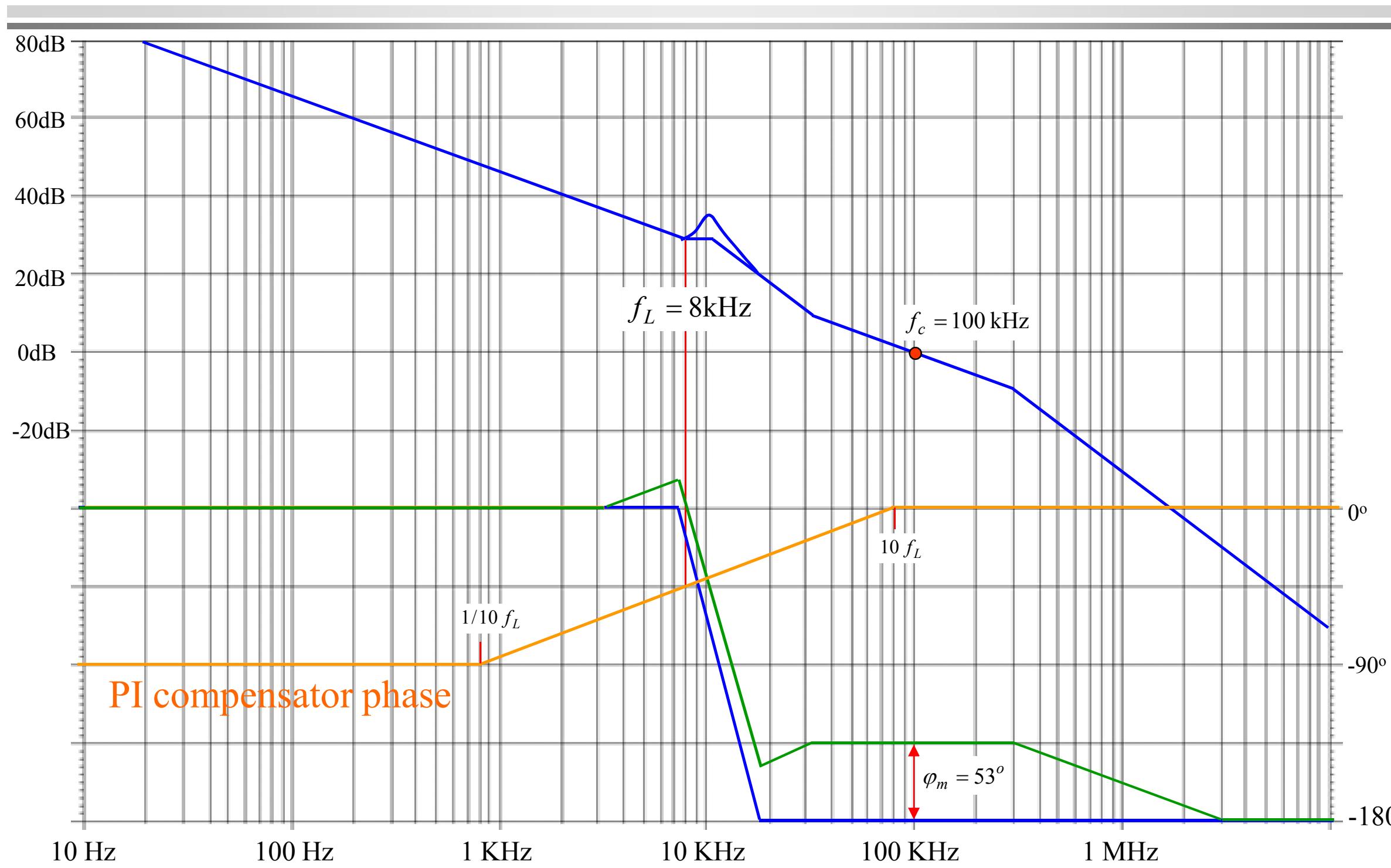


Complete analog PID compensator: summary

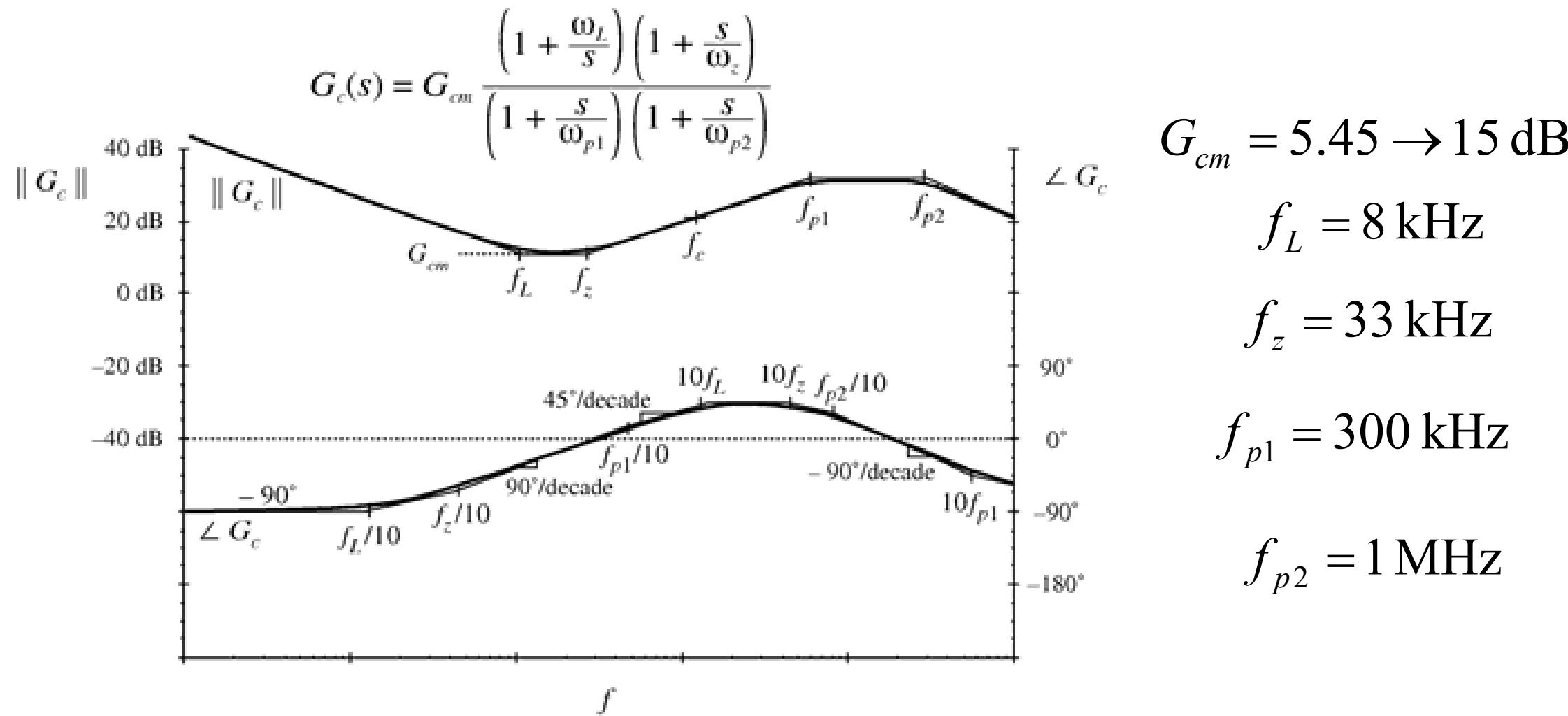


Crossover frequency: $f_c = 100 \text{ kHz}$ ($=1/10$ of f_s)

Phase margin: $\varphi_m = 53^\circ$

Magnitude and phase Bode plots of T

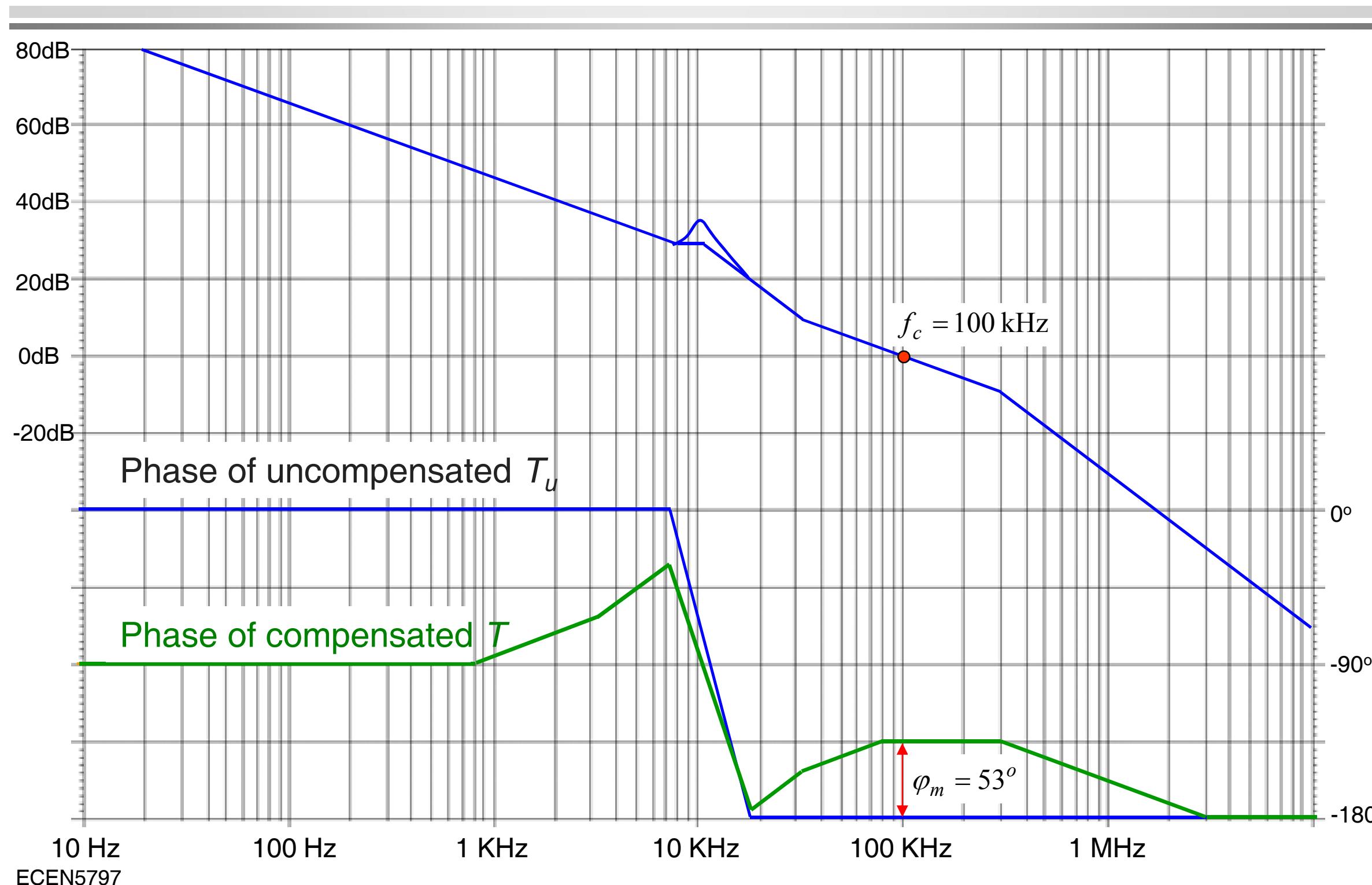

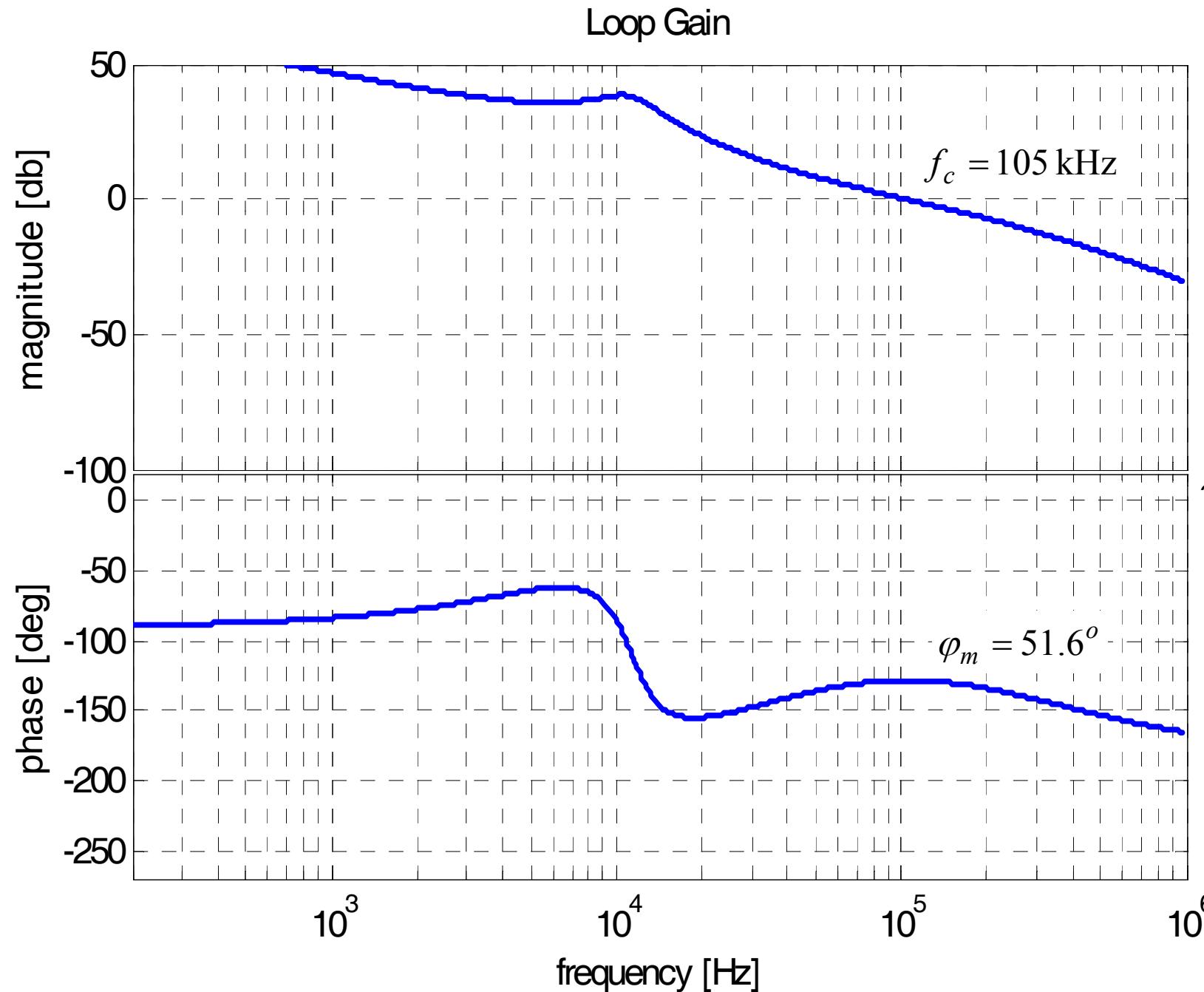Verification: exact loop gain magnitude and phase responses (MATLAB)



Verification of closed-loop responses

Closed-loop reference-to-output response

Closed-loop transfer function from \hat{v}_{ref} to $\hat{v}(s)$ is:


$$\frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \Bigg|_{\begin{array}{l} v_g = 0 \\ i_{load} = 0 \end{array}} = \frac{1}{H(s)} \frac{T(s)}{1 + T(s)}$$

Closed-loop output impedance


$$-\frac{\hat{v}(s)}{i_{load}(s)} \Bigg|_{\begin{array}{l} v_{ref} = 0 \\ v_g = 0 \end{array}} = \frac{Z_{out}(s)}{1 + T(s)}$$

and step-load transient response

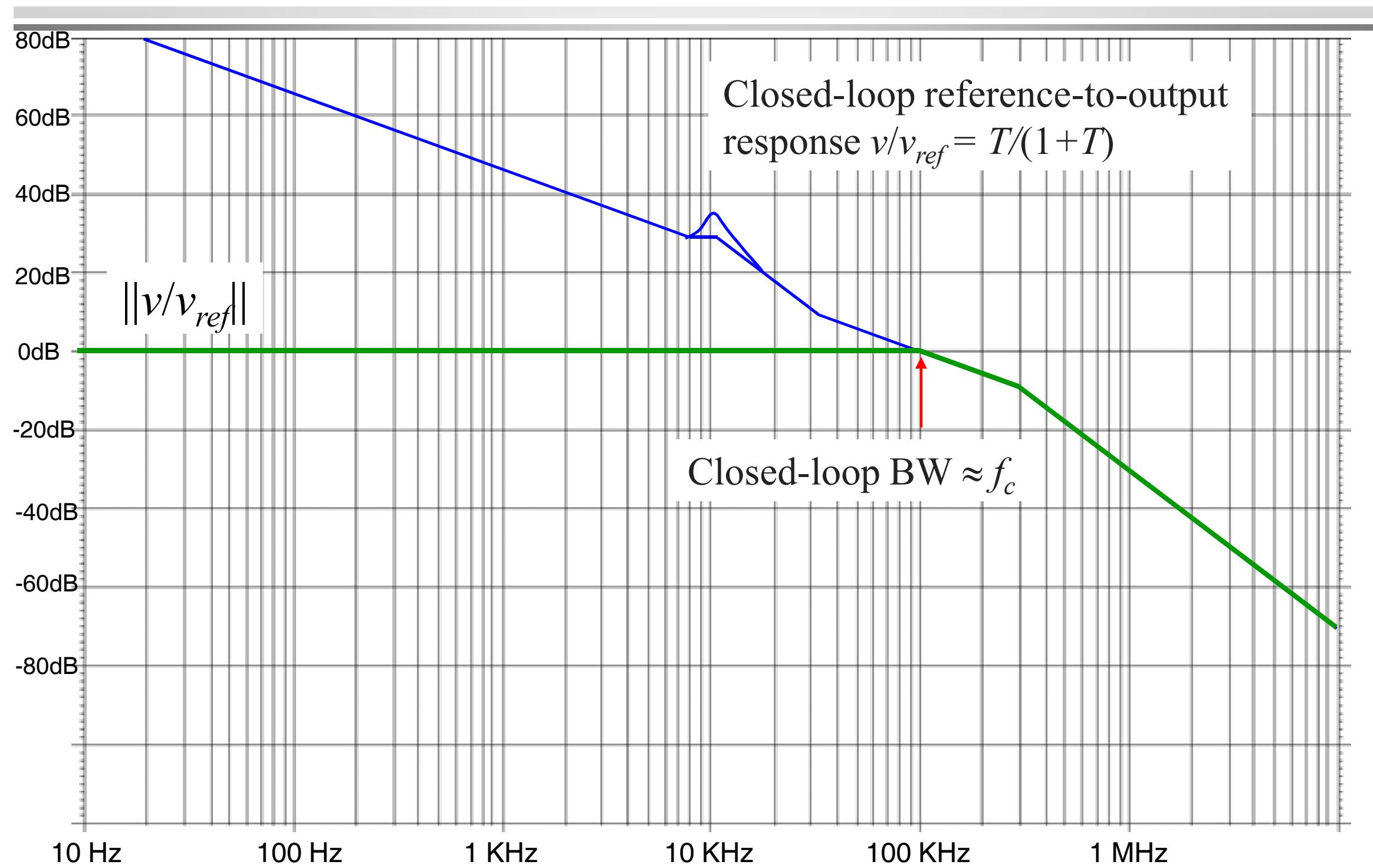
Construction of closed-loop $T/(1+T)$ response



Closed-loop reference-to-output response

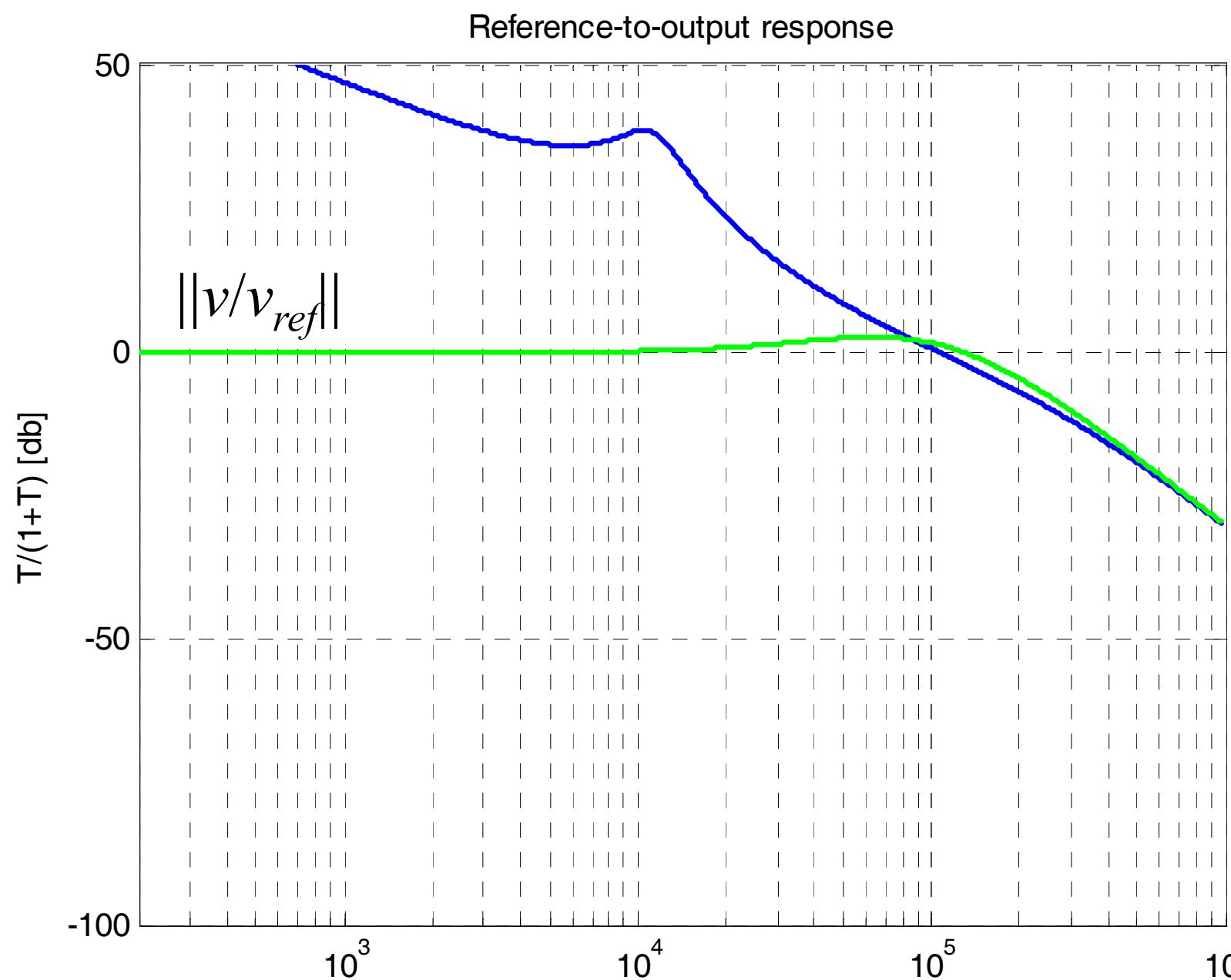


Small-signal step-reference response

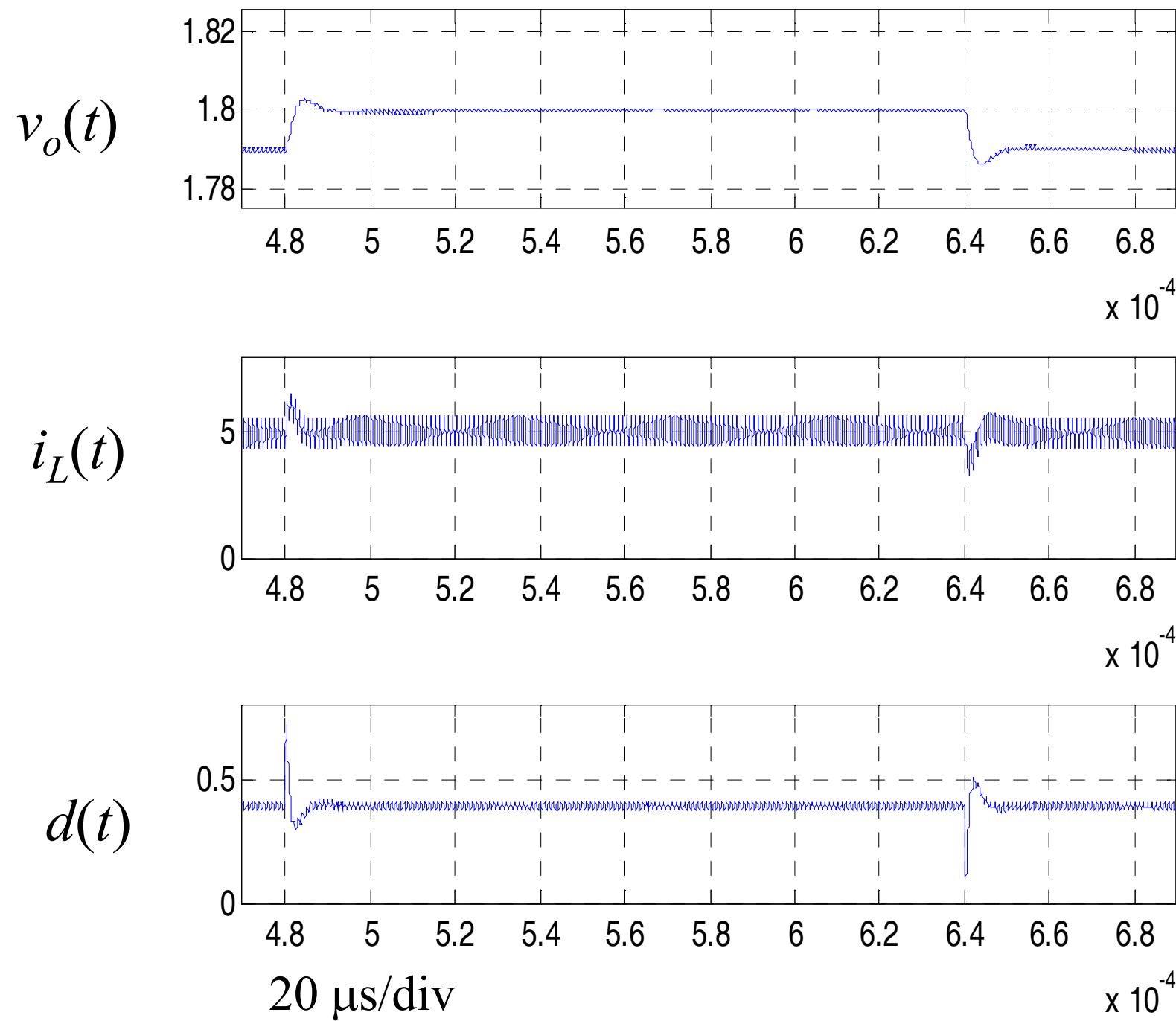


10 mV step
(1.79 V to 1.8 V)
in v_{ref}

Small-signal step-reference response

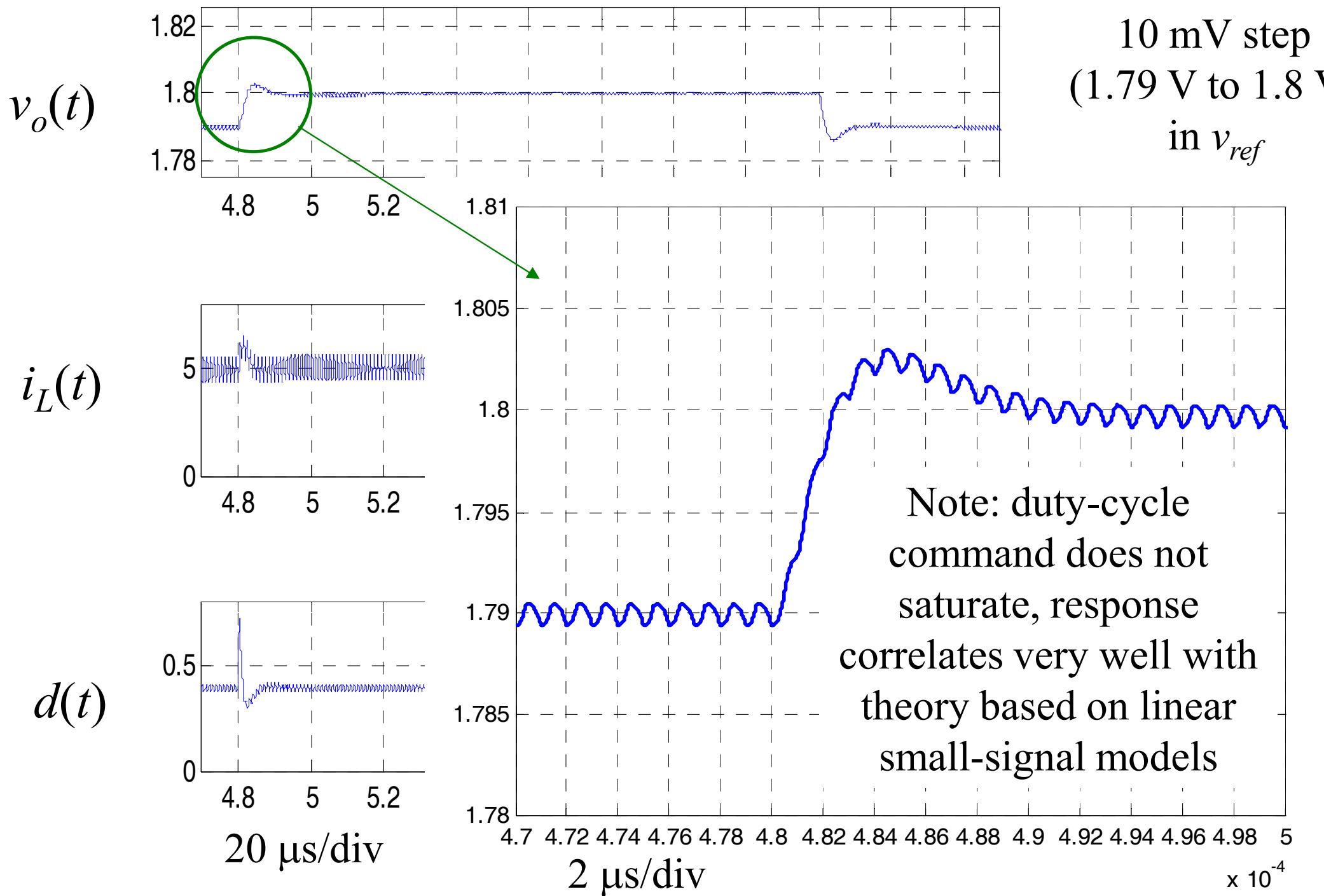

Output impedance

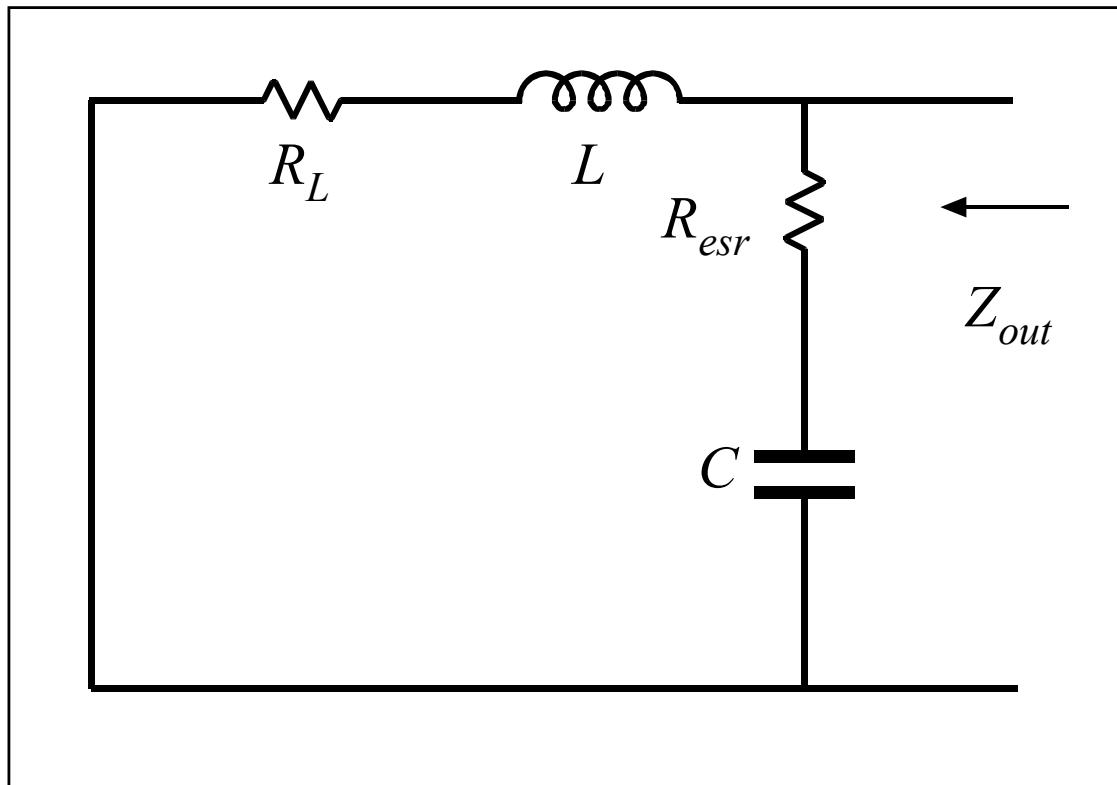
Synchronous buck open-loop output impedance




$$Z_{out}(s) = \left(R_{esr} + \frac{1}{sC} \right) \parallel (R_L + sL)$$

- $L = 1 \mu\text{H}$
- $R_L = 30 \text{ m}\Omega$
- $C = 200 \mu\text{F}$
- $R_{esr} = 0.8 \text{ m}\Omega$

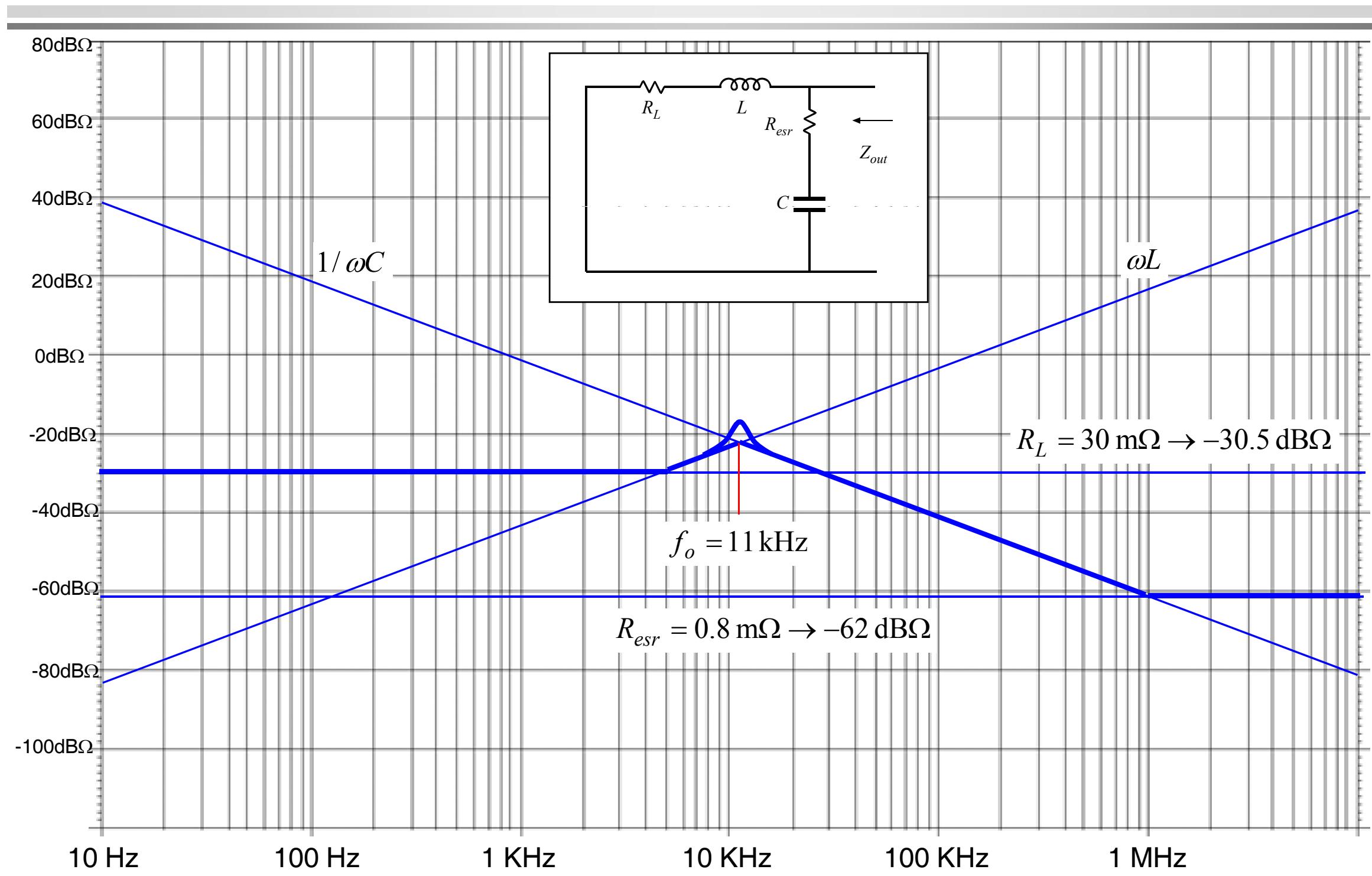
Open-loop output impedance: algebra on the graph




Construction of $1/(1+T)$

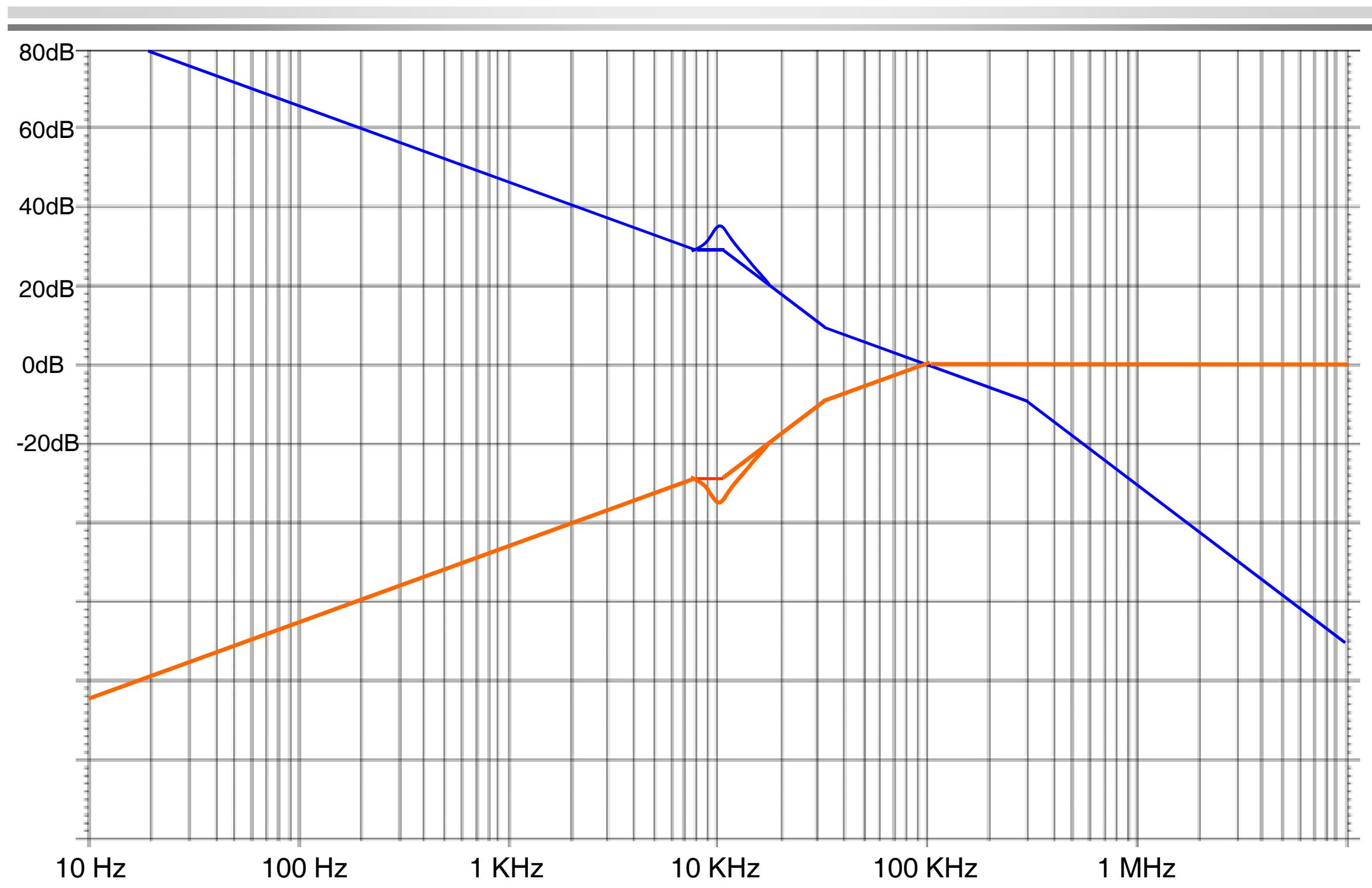

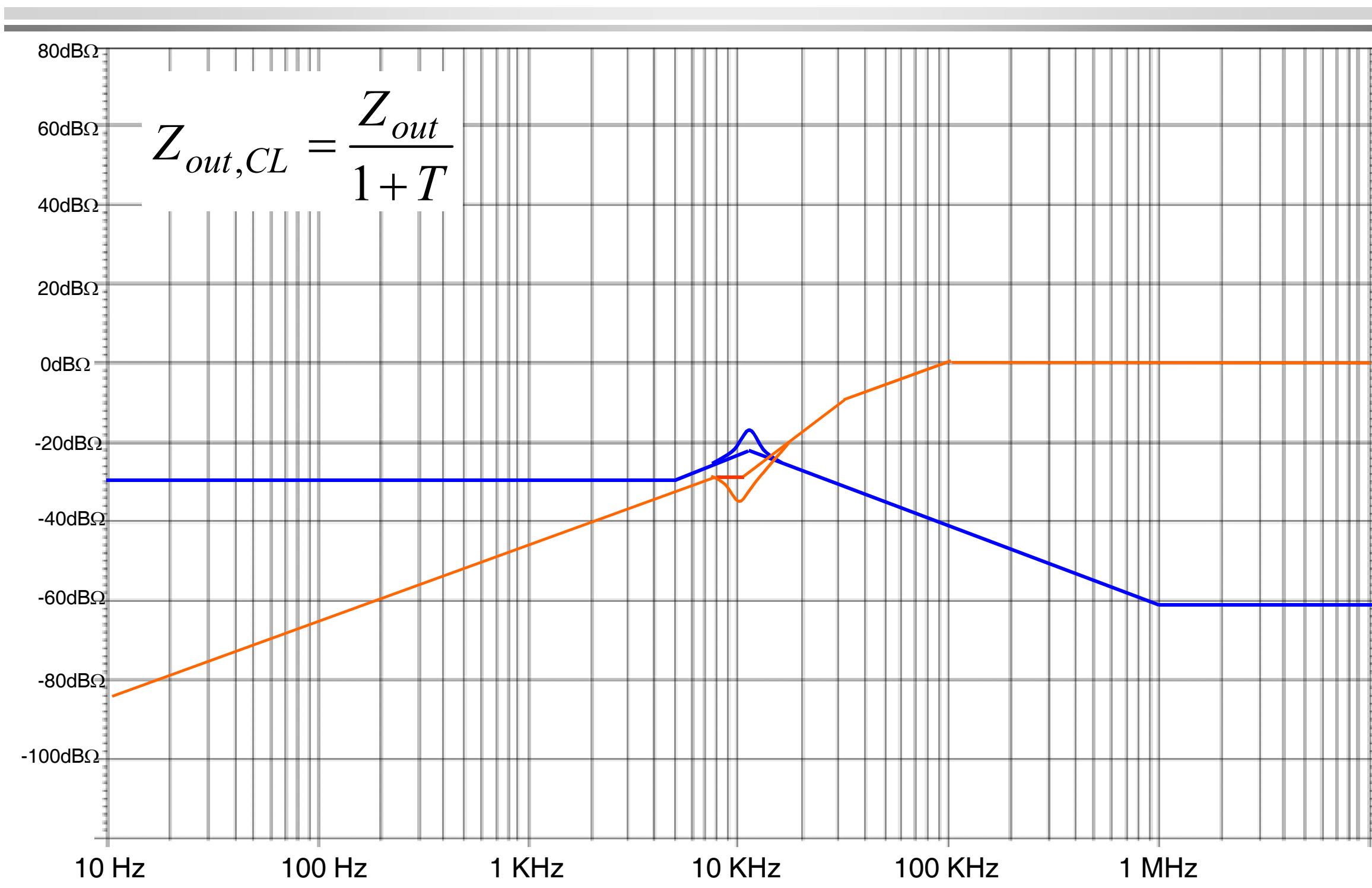
Construction of closed-loop output impedance



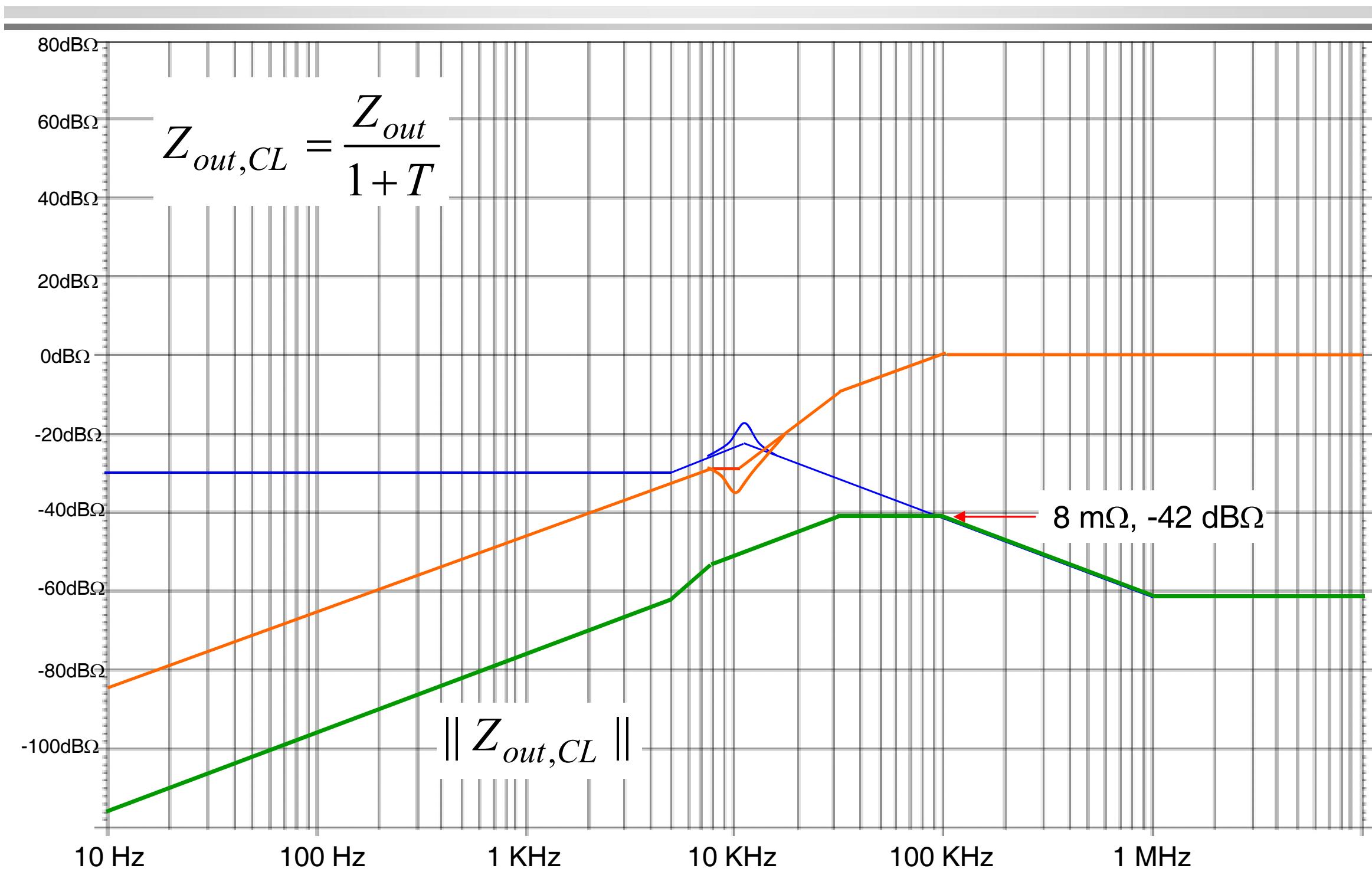
Closed-loop output impedance $Z_{out,CL}$



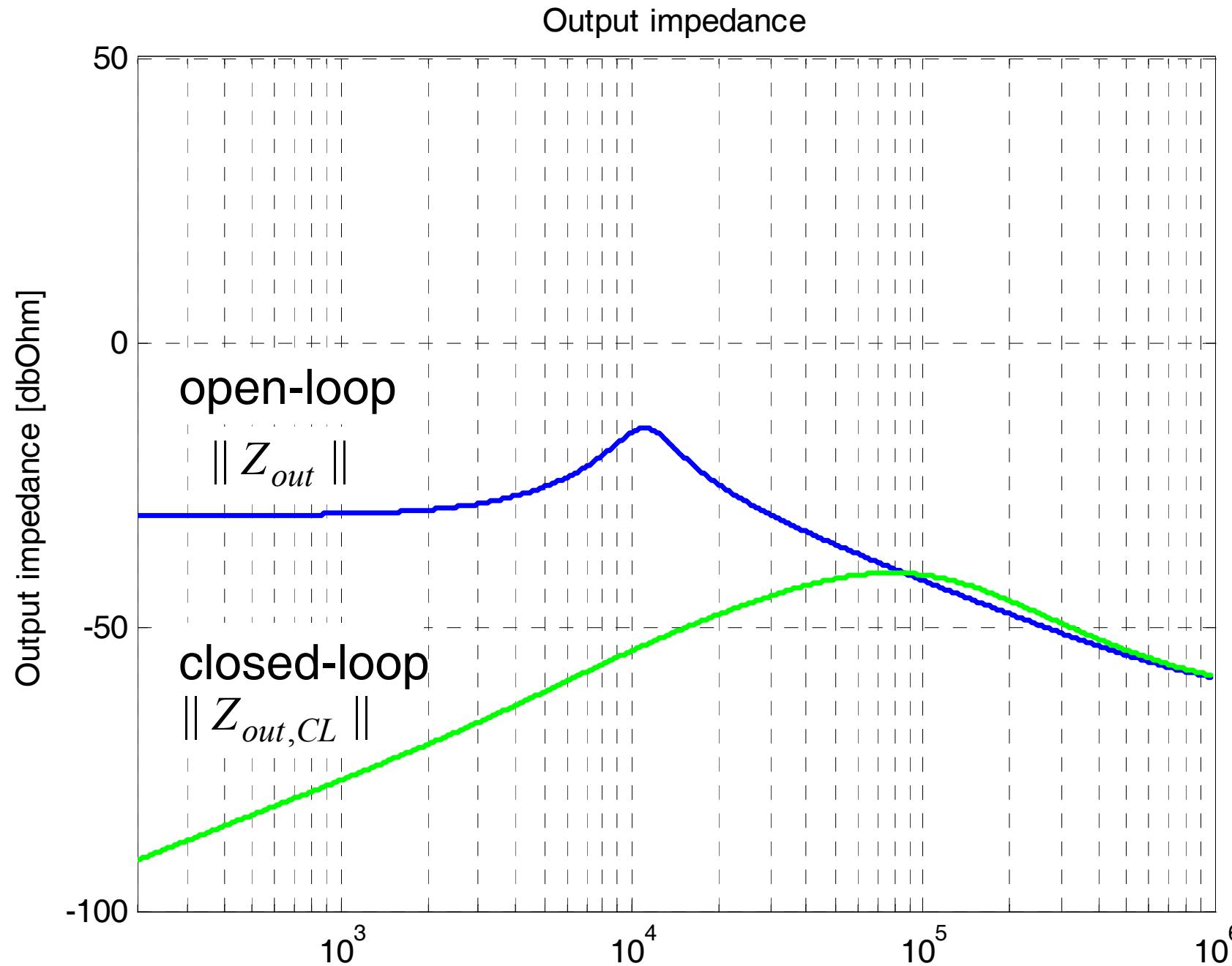Verification: closed-loop output impedance



Step-load transient responses

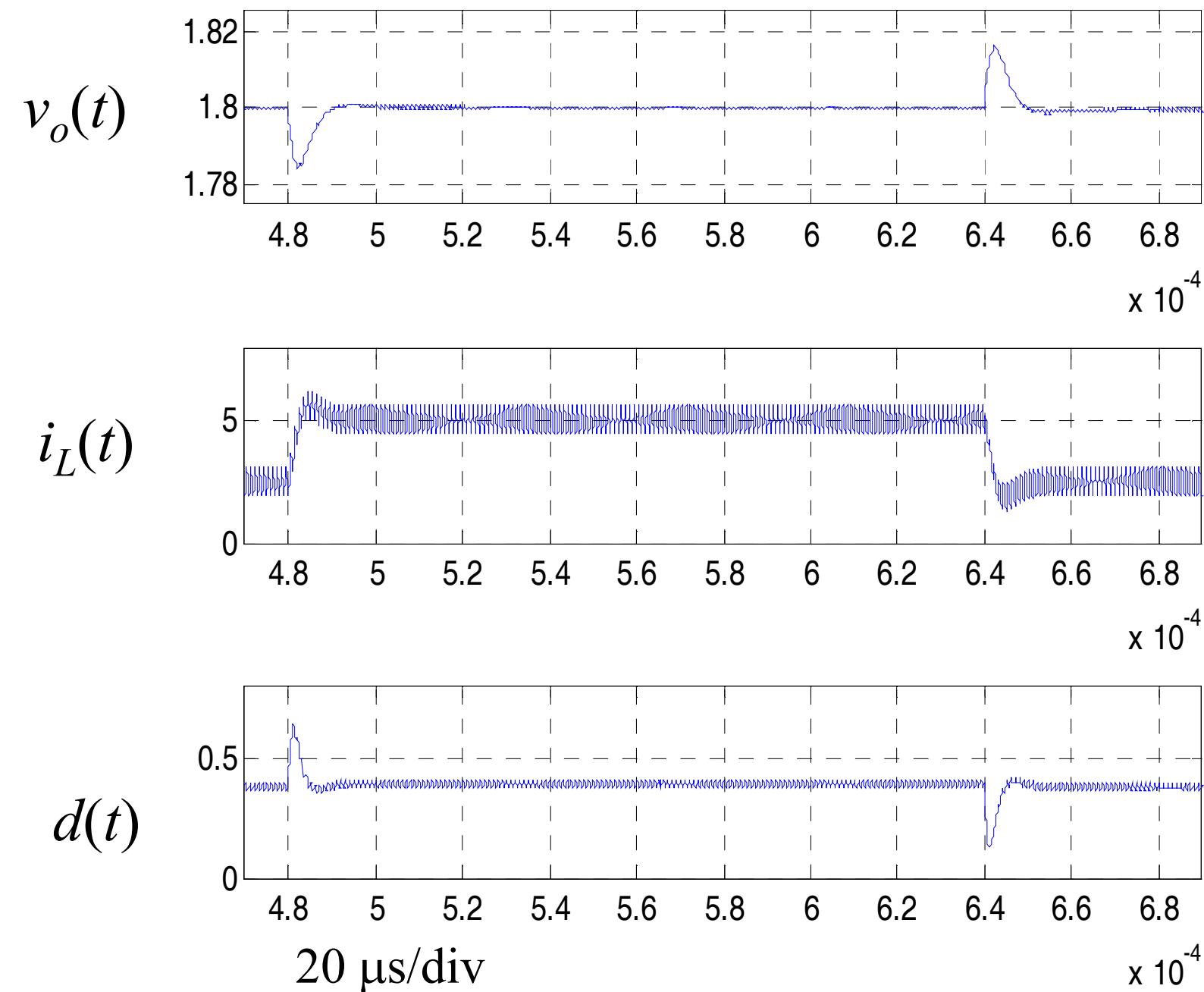

2.5-5 A step-load
transient

Step-load transient responses

